



Verilog HDL

Assignment 1

By: Magdy Ahmed Abbas Abdelhamid



Question 1

DESIGN HAS 7 INPUTS AND 2 OUTPUTS.

Verilog Code:

```
module in7out2 (A, B, C, D, E, F, Sel, Out, Out_Bar);  
  
input A, B, C, D, E, F, Sel;  
output Out, Out_Bar;  
  
wire AND1, XNOR1, MUX1;  
  
assign AND1 = (A & B & C);  
assign XNOR1 = ~(D ^ E ^ F);  
  
assign MUX1 = (Sel == 1)? XNOR1 : AND1;  
  
assign Out = MUX1;  
assign Out_Bar = ~MUX1;  
  
endmodule
```

Waveform:

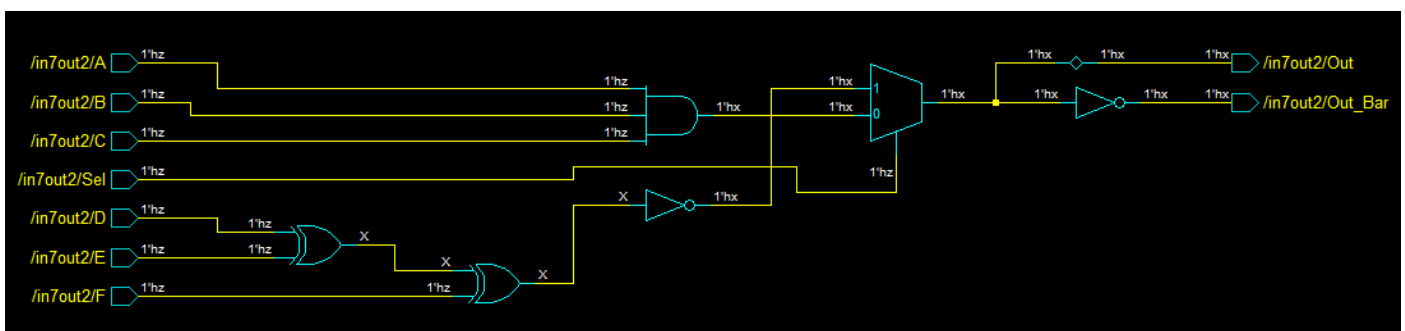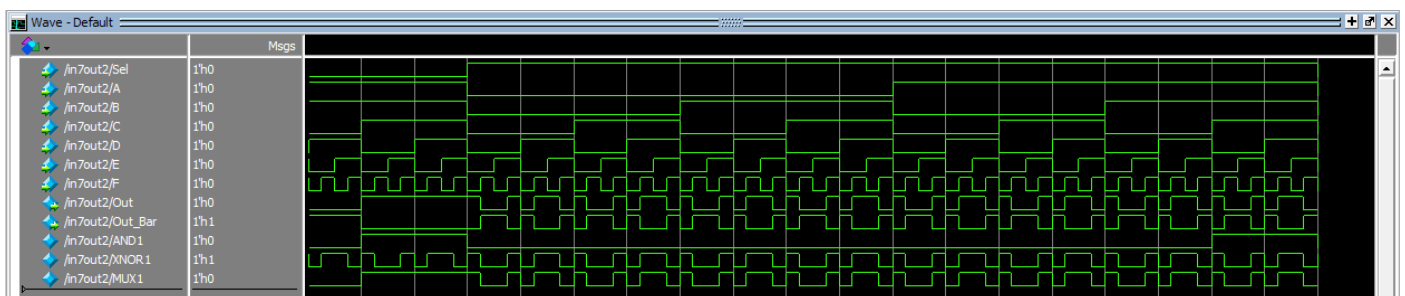


Question 2

4 - BIT ADDER USING ADDITION OPERATOR

Verilog Code:

```
module Halfadder4bit (A, B, C);  
  
input [3:0] A, B;  
output [3:0] C;  
  
assign C = A + B;  
  
endmodule
```

Waveform:

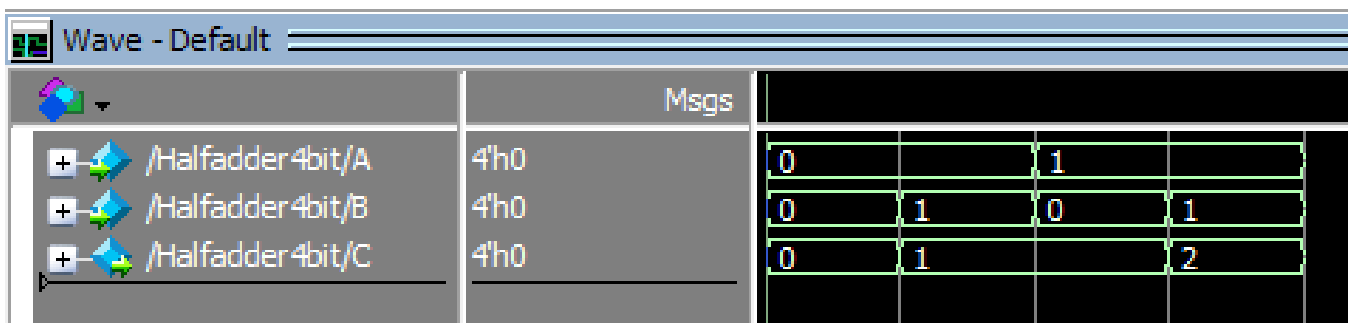



Question 3

4 - BIT ADDER USING THE BITWISE OPERATORS

Verilog Code:

```
module Fulladder4bit (A, B, Cin, S, Cout);  
  
input [3:0] A, B;  
input Cin;  
output [3:0] S;  
output Cout;  
  
wire and1, and2;  
  
assign and1 = A & B;  
assign and2 = (A ^ B) & Cin;  
assign S = A ^ B ^ Cin;  
assign Cout = and1 | and2;  
  
endmodule
```

Waveform:

 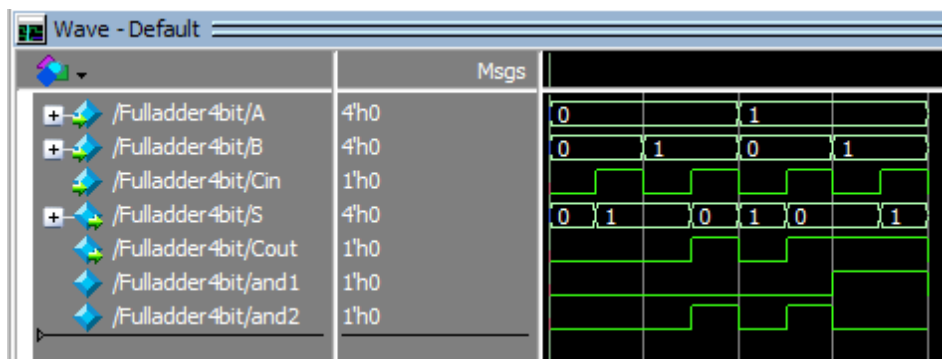

Question 4

2 × 4 DECODER USING CONDITIONAL OPERATOR


Verilog Code:

```
module Dec2to4(A, D);
input [1: 0] A;
output [3: 0] D;

assign D = (A == 2'b00)? 4'b0001 : (A == 2'b01)? 4'b0010 :
          (A == 2'b10)? 4'b0100 : 4'b1000;

endmodule
```

Waveform:

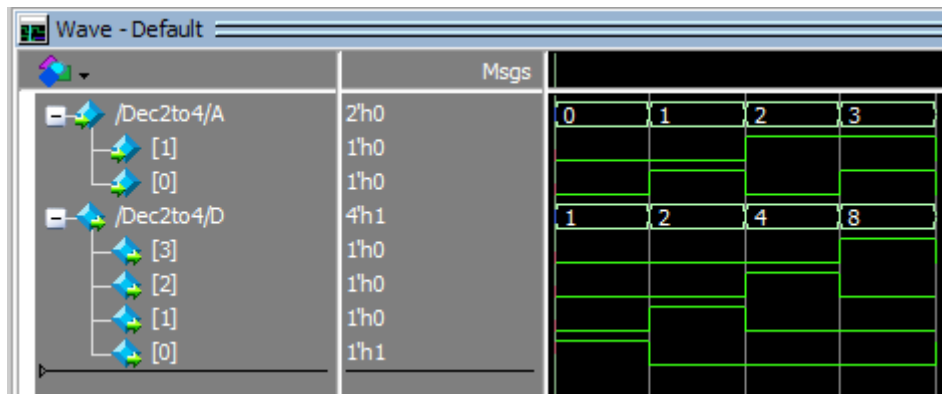

A ₁	A ₀	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Question 5

EVEN PARITY GENERATOR MODULE

Verilog Code:

```
module evenparity (A, out_with_parity);  
  
input [7:0] A;  
output [8:0] out_with_parity;  
  
assign out_with_parity = {A, ^A};  
  
endmodule
```

Waveform:

 

Question 6

COMPARATOR COMPARES 2 INPUTS USING CONDITIONAL OPERATOR

Verilog Code:

```
module comparator (A, B, ALTA, AGTB, AEQB);  
  
input [3:0] A, B;  
output ALTA, AGTB, AEQB;  
  
assign ALTA = (A < B)? 1'b1 : 1'b0;  
assign AGTB = (A > B)? 1'b1 : 1'b0;  
assign AEQB = (A == B)? 1'b1 : 1'b0;  
  
endmodule
```

Waveform:

