



Verilog HDL

Assignment 2

By: Magdy Ahmed Abbas Abdelhamid

Question 1

DESIGN HAS 5 INPUTS AND 2 OUTPUTS.

Verilog Code:

```
module in5out2 (D, A, B, C, Sel, Out, Out_Bar);  
  
input [2:0] D;  
input A, B, C, Sel;  
  
output reg Out, Out_Bar;  
  
reg AND2, OR1, XNOR1, MUX1;  
  
always @(*) begin  
    AND2 = D[1] & D[0];  
    OR1 = AND2 | D[2];  
    XNOR1 = ~(A ^ B ^ C);  
  
    if (Sel)  
        Out = XNOR1;  
    else  
        Out = OR1;  
    Out_Bar = ~Out;  
end  
  
endmodule
```

Testbench Code:

```
module in5out2_tb ();

reg [2:0] d;
reg a, b, c, sel, out_expected, out_expected_bar;
wire dut_out, dut_out_bar;


in5out2 DUT (.D(d), .A(a), .B(b), .C(c), .Sel(sel), .Out(dut_out), .Out_Bar(dut_out_bar));

integer i;
initial begin
    for (i = 0 ; i < 100; i = i + 1) begin
        d = $random;
        a = $random;
        b = $random;
        c = $random;
        sel = $random;
        out_expected = (sel == 1)? ~(a ^ b ^ c) : (d[0] & d[1]) | d[2];
        out_expected_bar = ~out_expected;
        #10;
        if (out_expected != dut_out) begin
            $display("The Design is Wrong!");
        end
        if (out_expected_bar != dut_out_bar) begin
            $display("The Design is Wrong!");
        end
    end
    $stop;
end


initial begin
    $monitor("D0 = %b,D1 = %b,D2 = %b,A = %b,B = %b,C = %b,OUT = %b,OUT_BAR\n\n= %b ", d[0], d[1], d[2], a, b, c, dut_out, dut_out_bar);
end

endmodule
```

Waveform:

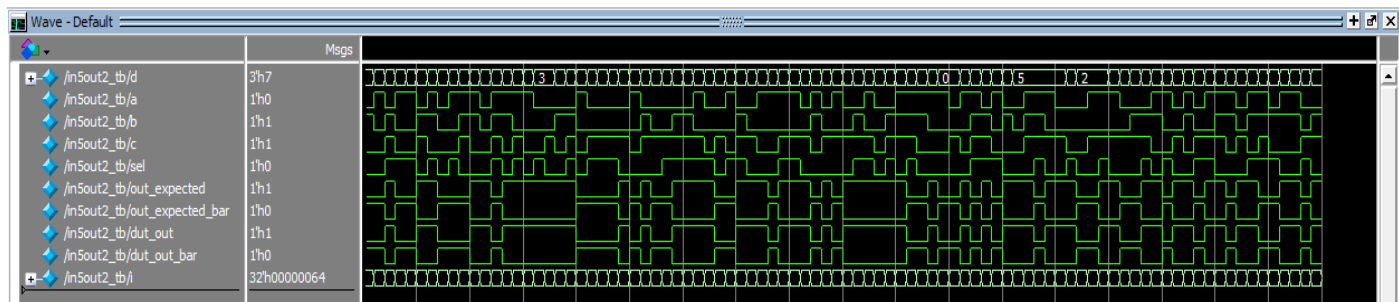

```
# D0 = 1, D1 = 1, D2 = 0, A = 0, B = 1, C = 1, OUT = 1, OUT_BAR = 0
# D0 = 0, D1 = 0, D2 = 1, A = 1, B = 1, C = 0, OUT = 1, OUT_BAR = 0
# D0 = 1, D1 = 0, D2 = 0, A = 1, B = 0, C = 0, OUT = 0, OUT_BAR = 1
# D0 = 1, D1 = 1, D2 = 0, A = 0, B = 0, C = 1, OUT = 1, OUT_BAR = 0
# D0 = 0, D1 = 0, D2 = 1, A = 1, B = 1, C = 0, OUT = 1, OUT_BAR = 0
# D0 = 1, D1 = 0, D2 = 0, A = 0, B = 0, C = 1, OUT = 0, OUT_BAR = 1
# D0 = 0, D1 = 1, D2 = 1, A = 1, B = 0, C = 1, OUT = 1, OUT_BAR = 0
# D0 = 0, D1 = 0, D2 = 1, A = 1, B = 1, C = 1, OUT = 1, OUT_BAR = 0
# D0 = 1, D1 = 0, D2 = 0, A = 1, B = 1, C = 0, OUT = 0, OUT_BAR = 1
# D0 = 1, D1 = 1, D2 = 0, A = 0, B = 0, C = 1, OUT = 1, OUT_BAR = 0
# D0 = 0, D1 = 0, D2 = 0, A = 1, B = 1, C = 0, OUT = 1, OUT_BAR = 0
# D0 = 0, D1 = 1, D2 = 1, A = 1, B = 1, C = 1, OUT = 0, OUT_BAR = 1
# D0 = 0, D1 = 0, D2 = 0, A = 0, B = 1, C = 0, OUT = 0, OUT_BAR = 1
# D0 = 0, D1 = 1, D2 = 1, A = 1, B = 1, C = 0, OUT = 1, OUT_BAR = 0
# D0 = 1, D1 = 1, D2 = 1, A = 1, B = 1, C = 0, OUT = 1, OUT_BAR = 0
# D0 = 1, D1 = 0, D2 = 1, A = 0, B = 0, C = 1, OUT = 0, OUT_BAR = 1
# D0 = 1, D1 = 1, D2 = 1, A = 0, B = 1, C = 1, OUT = 1, OUT_BAR = 0
```

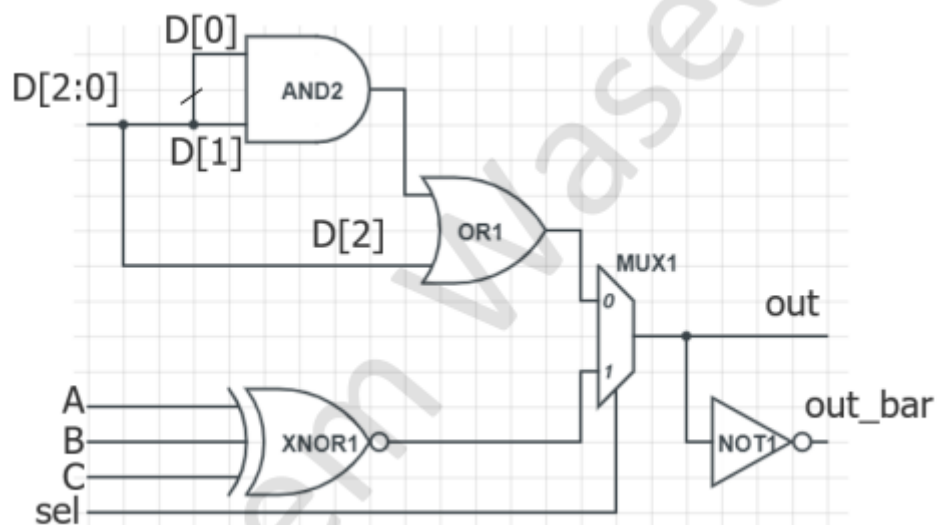

Question 2

DESIGN 4 - BIT PRIORITY ENCODER

Verilog Code:

```
module priorityencoder (X, Y);  
  
input [3:0] X;  
output reg [1:0] Y;  
  
always @(X) begin  
    if (X[3])  
        Y = 2'b11;  
    else  
        if (X[2])  
            Y = 2'b10;  
        else  
            if (X[1])  
                Y = 2'b01;  
            else  
                Y = 2'b00;  
    end  
  
endmodule  
/*  
module priorityencoder (X, Y);  
  
input [3:0] X;  
output reg [1:0] Y;  
  
always @(X) begin  
    casex (X)  
        4'b1xxx : Y = 2'b11;  
        4'b01xx : Y = 2'b10;  
        4'b001x : Y = 2'b01;  
        4'b000x : Y = 2'b00;  
    endcase  
end  
endmodule  
*/
```

Testbench Code:

```
module priorityencoder_tb ();

reg [3:0] x_dut;
reg [1:0] y_expected;
wire [1:0] y_dut;

priorityencoder DUT (.X(x_dut),.Y(y_dut));


integer i;
initial begin
    for (i = 0 ; i < 100 ; i = i + 1) begin
        x_dut = $random;

        casex (x_dut)
            4'b1xxx : y_expected = 2'b11;
            4'b01xx : y_expected = 2'b10;
            4'b001x : y_expected = 2'b01;
            4'b000x : y_expected = 2'b00;
        endcase
        #10;
        if (y_dut != y_expected) begin
            $display("The Design is Wrong!");
            $stop;
        end
    end
    $stop;
end

initial begin
    $monitor("X3 X2 X1 X0 = %b,Y1 Y0 = %b ",x_dut,y_dut);
end

endmodule
```

Waveform:

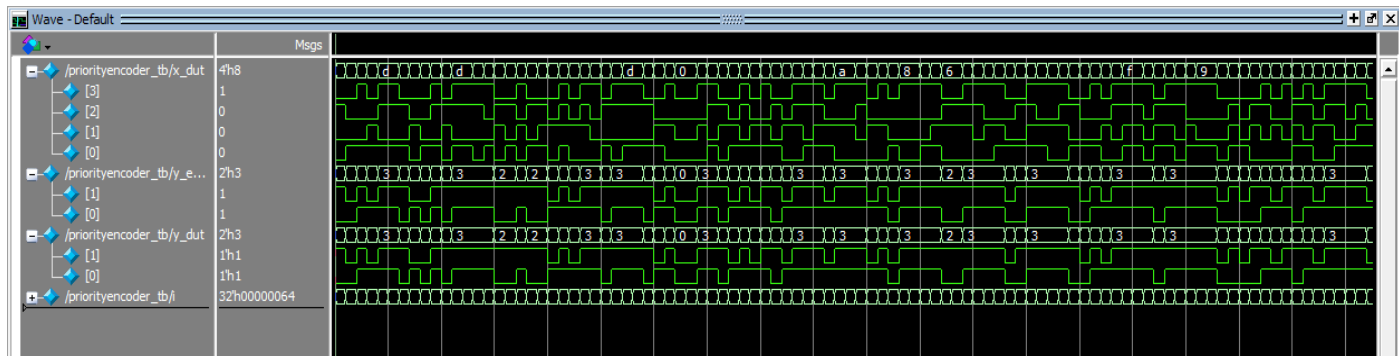

```
# X3 X2 X1 X0 = 0000, Y1 Y0 = 00
# X3 X2 X1 X0 = 0111, Y1 Y0 = 10
# X3 X2 X1 X0 = 0001, Y1 Y0 = 00
# X3 X2 X1 X0 = 0110, Y1 Y0 = 10
# X3 X2 X1 X0 = 1100, Y1 Y0 = 11
# X3 X2 X1 X0 = 0010, Y1 Y0 = 01
# X3 X2 X1 X0 = 1000, Y1 Y0 = 11
# X3 X2 X1 X0 = 0111, Y1 Y0 = 10
# X3 X2 X1 X0 = 1101, Y1 Y0 = 11
# X3 X2 X1 X0 = 0010, Y1 Y0 = 01
# X3 X2 X1 X0 = 1110, Y1 Y0 = 11
# X3 X2 X1 X0 = 1101, Y1 Y0 = 11
# X3 X2 X1 X0 = 1001, Y1 Y0 = 11
# X3 X2 X1 X0 = 1111, Y1 Y0 = 11
# X3 X2 X1 X0 = 0011, Y1 Y0 = 01
# X3 X2 X1 X0 = 0101, Y1 Y0 = 10
# X3 X2 X1 X0 = 1000, Y1 Y0 = 11
```

x3	x2	x1	x0	y1	y0
1	X	X	X	1	1
0	1	X	X	1	0
0	0	1	X	0	1
0	0	0	X	0	0

Question 3

DESIGN A DECIMAL TO BCD ENCODER

Verilog Code:

```
module BCD_enc (D, Y);  
  
input [9:0] D;  
output reg [3:0] Y;  
  
always @(*) begin  
    case (D)  
        10'b0000000001 : Y = 4'b0000;  
        10'b0000000010 : Y = 4'b0001;  
        10'b0000000100 : Y = 4'b0010;  
        10'b0000001000 : Y = 4'b0011;  
        10'b0000010000 : Y = 4'b0100;  
        10'b0000100000 : Y = 4'b0101;  
        10'b0001000000 : Y = 4'b0110;  
        10'b0010000000 : Y = 4'b0111;  
        10'b0100000000 : Y = 4'b1000;  
        10'b1000000000 : Y = 4'b1001;  
        default : Y = 4'b0000;  
    endcase  
end  
  
endmodule
```


Testbench Code:

```
module BCD_enc_tb ();

reg [9:0] d;
wire [3:0] y_dut;
BCD_enc DUT (.D(d),.Y(y_dut));
reg [9:0] temp;


integer i;
initial begin
    d = $random;
    temp = d;
    for (i = 0 ; i < 10 ; i = i + 1) begin
        d = temp << i;
        #10;
    end
    $stop;
end

initial begin
    $monitor("D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = %b,
              Y2 Y1 Y0 = %b ",d,y_dut);
end

endmodule
```

Waveform:



```
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 0100100100, Y2 Y1 Y0 = 0000
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 1001001000, Y2 Y1 Y0 = 0000
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 0010010000, Y2 Y1 Y0 = 0000
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 0100100000, Y2 Y1 Y0 = 0000
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 1001000000, Y2 Y1 Y0 = 0000
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 0010000000, Y2 Y1 Y0 = 0111
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 0100000000, Y2 Y1 Y0 = 1000
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 1000000000, Y2 Y1 Y0 = 1001
# D9 D8 D7 D6 D5 D4 D3 D2 D1 D0 = 0000000000, Y2 Y1 Y0 = 0000
```

Input										Output			
D ₉	D ₈	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀	Y ₃	Y ₂	Y ₁	Y ₀
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	0	0	0	0	1
0	0	0	0	0	0	0	1	0	0	0	0	1	0
0	0	0	0	0	0	1	0	0	0	0	0	1	1
0	0	0	0	0	1	0	0	0	0	0	1	0	0
0	0	0	0	1	0	0	0	0	0	0	1	0	1
0	0	0	1	0	0	0	0	0	0	0	1	1	0
0	0	1	0	0	0	0	0	0	0	0	1	1	1
0	1	0	0	0	0	0	0	0	0	1	0	0	0
1	0	0	0	0	0	0	0	0	0	1	0	0	1

Question 4

N - BIT ADDER USING DATAFLOW

Verilog Code:

```
module NbitAdder (A, B, C);  
  
    parameter N = 1;  
    input [N - 1 : 0] A, B;  
    output [N - 1 : 0] C;  
  
    assign C = A + B;  
  
endmodule
```

Testbench Code:

```
module NbitAdder_tb ();

parameter n = 2;
reg [n - 1 : 0] a_tb, b_tb, c_expected;
wire [n - 1 : 0] c_dut;

NbitAdder #(.N(n)) DUT (.A(a_tb), .B(b_tb), .C(c_dut));


integer i;
initial begin

    // Directed Testing
    #0 a_tb = 0; b_tb = 1; c_expected = 1;
    #10 a_tb = 1; b_tb = 2; c_expected = 3;
    #10 a_tb = 1; b_tb = 7; c_expected = 8;
    #10 a_tb = 5; b_tb = 4; c_expected = 9;
    #10;
    // Randomized Testing
    for (i = 0; i < 100; i = i + 1) begin
        a_tb = $random;
        b_tb = $random;
        c_expected = a_tb + b_tb;
        #10;
        if (c_dut != c_expected) begin
            $display("The Nbit Adder Design is Wrong!");
            $stop;
        end
    end
    $stop;
end

initial begin
    $monitor("A = %b, B = %b, C_DUT = %b, C_Expected = %b ", a_tb, b_tb, c_dut, c_expected);
end

endmodule
```

Waveform:

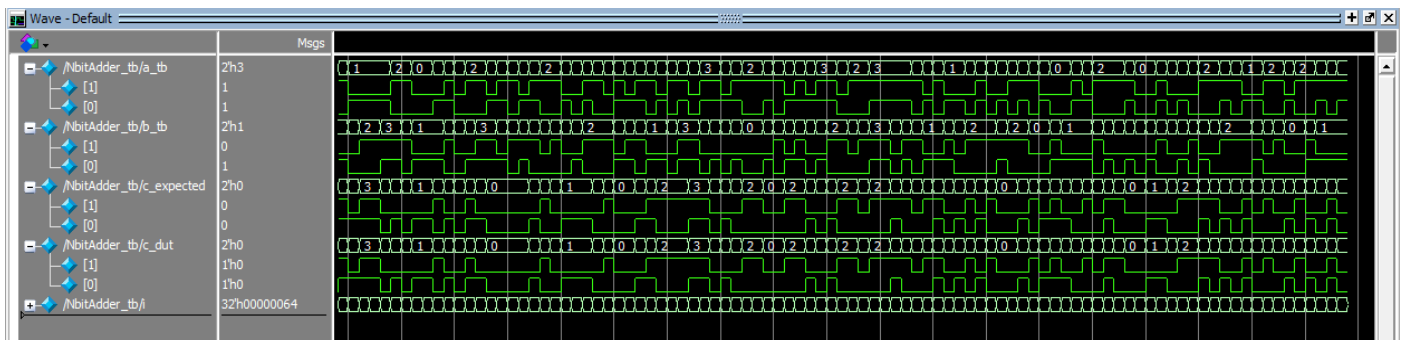

```
# A = 00, B = 10, C_DUT = 10, C_Expected = 10
# A = 10, B = 00, C_DUT = 10, C_Expected = 10
# A = 10, B = 10, C_DUT = 00, C_Expected = 00
# A = 11, B = 11, C_DUT = 10, C_Expected = 10
# A = 11, B = 00, C_DUT = 11, C_Expected = 11
# A = 11, B = 11, C_DUT = 10, C_Expected = 10
# A = 10, B = 10, C_DUT = 00, C_Expected = 00
# A = 01, B = 01, C_DUT = 10, C_Expected = 10
# A = 10, B = 01, C_DUT = 11, C_Expected = 11
# A = 01, B = 11, C_DUT = 00, C_Expected = 00
# A = 01, B = 00, C_DUT = 01, C_Expected = 01
# A = 00, B = 10, C_DUT = 10, C_Expected = 10
# A = 11, B = 10, C_DUT = 01, C_Expected = 01
# A = 00, B = 10, C_DUT = 10, C_Expected = 10
# A = 01, B = 11, C_DUT = 00, C_Expected = 00
# A = 10, B = 10, C_DUT = 00, C_Expected = 00
# A = 11, B = 10, C_DUT = 01, C_Expected = 01
# A = 10, B = 00, C_DUT = 10, C_Expected = 10
# A = 01, B = 00, C_DUT = 01, C_Expected = 01
# A = 00, B = 11, C_DUT = 11, C_Expected = 11
# A = 00, B = 01, C_DUT = 01, C_Expected = 01
# A = 11, B = 01, C_DUT = 00, C_Expected = 00
```

Question 5

DESIGN N - BIT ALU

Verilog Code:

```
module NbitALU (A, B, OPCODE, RESULT);

parameter M = 1;
input [M - 1 : 0] A, B;
input [1 : 0] OPCODE;
output reg [M - 1 : 0] RESULT;

wire [M - 1 : 0] adder_out;

NbitAdder #(.N(M)) Addition(.A(A), .B(B), .C(adder_out));

always @(*) begin
    case (OPCODE)
        2'b00 : RESULT = adder_out;
        2'b10 : RESULT = A - B;
        2'b01 : RESULT = A | B;
        2'b11 : RESULT = A ^ B;
    endcase
end

endmodule
```

Testbench Code:

```
module NbitALU_tb ();


parameter n = 1;
reg [n - 1 : 0] a_tb, b_tb;
reg [n - 1 : 0] result_expected;
reg [1 : 0] opcode_tb;
wire [n - 1 : 0] result_dut;

NbitALU #(.M(n)) DUT
(.A(a_tb),.B(b_tb),.OPCODE(opcode_tb),.RESULT(result_dut));

integer i;
initial begin
    for (i = 0 ; i < 100 ; i = i + 1) begin
        a_tb = $random;
        b_tb = $random;
        opcode_tb = $random;
        case (opcode_tb)
            2'b00 : result_expected = a_tb + b_tb;
            2'b10 : result_expected = a_tb - b_tb;
            2'b01 : result_expected = a_tb | b_tb;
            2'b11 : result_expected = a_tb ^ b_tb;
        endcase
        #10;
        if (result_dut != result_expected) begin
            $display ("The ALU Design is Wrong! ");
            $stop;
        end
    end
    $stop;
End
initial begin
    $monitor("A = %b,B = %b,Opcode = %b,
              Result = %b ",a_tb,b_tb,opcode_tb,result_dut);
end


endmodule
```

Waveform:

 

```
# A = 0, B = 0, Opcode = 10, Result = 0
# A = 0, B = 1, Opcode = 00, Result = 1
# A = 0, B = 0, Opcode = 01, Result = 0
# A = 1, B = 0, Opcode = 11, Result = 1
# A = 1, B = 1, Opcode = 01, Result = 1
# A = 0, B = 1, Opcode = 11, Result = 1
# A = 1, B = 0, Opcode = 10, Result = 1
# A = 1, B = 0, Opcode = 00, Result = 1
# A = 1, B = 1, Opcode = 10, Result = 0
# A = 0, B = 1, Opcode = 00, Result = 1
# A = 0, B = 1, Opcode = 10, Result = 1
# A = 1, B = 1, Opcode = 00, Result = 0
# A = 1, B = 0, Opcode = 11, Result = 1
# A = 0, B = 0, Opcode = 11, Result = 0
# A = 0, B = 0, Opcode = 00, Result = 0
# A = 1, B = 1, Opcode = 01, Result = 1
# A = 1, B = 1, Opcode = 00, Result = 0
# A = 1, B = 1, Opcode = 11, Result = 0
# A = 0, B = 0, Opcode = 10, Result = 0
# A = 1, B = 1, Opcode = 01, Result = 1
```

Inputs		Outputs
opcode		Operation
0	0	Addition
1	0	Subtraction
0	1	OR
1	1	XOR

 

Question 6

4 - BIT ALU DISPLAY ON 7 SEGMENT LED DISPLAY

Verilog Code:

```
module ALU4bit7SegmentLED (A, B, Opcode, enable, a, b, c, d, e, f, g);
parameter N = 1;
input [N - 1 : 0] A, B;
input [1: 0] Opcode;
input enable;
output reg a, b, c, d, e, f, g;
wire [N - 1 : 0] Result;
reg [6: 0] LEDs;
NbitALU #(. M(N)) ALU(. A(A), . B(B), . OPCODE(Opcode), . RESULT(Result));
always @(*) begin
    if (enable) begin
        case (Result)
            4'h0 : LEDs = 7'b111_1110; // LEDS = {a, b, c, d, e, f, g}
            4'h1 : LEDs = 7'b011_0000;
            4'h2 : LEDs = 7'b110_1101;
            4'h3 : LEDs = 7'b111_1001;
            4'h4 : LEDs = 7'b011_0011;
            4'h5 : LEDs = 7'b101_1011;
            4'h6 : LEDs = 7'b101_1111;
            4'h7 : LEDs = 7'b111_0000;
            4'h8 : LEDs = 7'b111_1111;
            4'h9 : LEDs = 7'b111_1011;
            4'hA : LEDs = 7'b111_0111;
            4'hB : LEDs = 7'b001_1111;
            4'hC : LEDs = 7'b100_1110;
            4'hD : LEDs = 7'b011_1101;
            4'hE : LEDs = 7'b100_1111;
            4'hF : LEDs = 7'b100_0111;
        endcase
    end else LEDs = 7'b000_0000;
end
always @(*) begin
    a = LEDs[6];
    b = LEDs[5];
    c = LEDs[4];
    d = LEDs[3];
    e = LEDs[2];
    f = LEDs[1];
    g = LEDs[0];
end endmodule
```

Testbench Code:

```
module ALU4bit7SegmentLED_tb ();

parameter n = 1;
reg [n - 1 : 0] A_tb, B_tb;
reg [1: 0] Op_code;
reg Enable;
wire a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb;
reg a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp;
reg [n - 1 : 0] Result_Expected;

ALU4bit7SegmentLED #(N(n)) DUT (A_tb, B_tb, Op_code, Enable, a_tb, b_tb, c_tb, d_tb, e_tb, f_tb, g_tb);

integer i;
initial begin
    for (i = 0 ; i < 100 ; i = i + 1) begin
        A_tb = $random;
        B_tb = $random;
        Op_code = $random;
        Enable = $random;
        case (Op_code)
            2'b00 : Result_Expected = A_tb + B_tb;
            2'b10 : Result_Expected = A_tb - B_tb;
            2'b01 : Result_Expected = A_tb | B_tb;
            2'b11 : Result_Expected = A_tb ^ B_tb;
        endcase
        if (Enable) begin
            case (Result_Expected)
                // {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = {a, b, c, d, e, f, g}
                4'h0 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b111_1110;
                4'h1 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b011_0000;
                4'h2 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b110_1101;
                4'h3 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b111_1001;
                4'h4 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b011_0011;
                4'h5 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b101_1011;
                4'h6 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b101_1111;
                4'h7 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b111_0000;
                4'h8 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b111_1111;
                4'h9 : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b111_1011;
                4'hA : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b111_0111;
                4'hB : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b001_1111;
                4'hC : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b100_1110;
                4'hD : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b011_1101;
                4'hE : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b100_1111;
                4'hF : {a_tb_Exp, b_tb_Exp, c_tb_Exp, d_tb_Exp, e_tb_Exp, f_tb_Exp, g_tb_Exp} = 7'b100_0111;
            endcase
        end
    end
end
```

```

else
    {a_tb_Exp,b_tb_Exp,c_tb_Exp,d_tb_Exp,e_tb_Exp,f_tb_Exp,g_tb_Exp} = 7'b000_0000;
#10;
if ({a_tb_Exp,b_tb_Exp,c_tb_Exp,d_tb_Exp,e_tb_Exp,f_tb_Exp,g_tb_Exp} !
    = {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb}) begin
    $display("The ALU 4 bit 7 Segment LEDs Design is Wrong!");
    $stop;
end
end
end
$stop;
end


initial begin
    $monitor("Digit = %d, abcdefg = %b ", Result_Expected, {a_tb,b_tb,c_tb,d_tb,e_tb,f_tb,g_tb});
end

endmodule


```

	Input		Output					
Digit	enable	a	b	c	d	e	f	g
0	1	1	1	1	1	1	1	0
1	1	0	1	1	0	0	0	0
2	1	1	1	0	1	1	0	1
3	1	1	1	1	1	0	0	1
4	1	0	1	1	0	0	1	1
5	1	1	0	1	1	0	1	1
6	1	1	0	1	1	1	1	1
7	1	1	1	1	0	0	0	0
8	1	1	1	1	1	1	1	1
9	1	1	1	1	1	0	1	1
A	1	1	1	1	0	1	1	1
b	1	0	0	1	1	1	1	1
C	1	1	0	0	1	1	1	0
d	1	0	1	1	1	1	0	1
E	1	1	0	0	1	1	1	1
F	1	1	0	0	0	1	1	1
x	0	0	0	0	0	0	0	0

Waveform:

 

```
# Digit = 1, abcdefg = 0000000
# Digit = 1, abcdefg = 0110000
# Digit = 0, abcdefg = 0000000
# Digit = 0, abcdefg = 1111110
# Digit = 1, abcdefg = 0000000
# Digit = 0, abcdefg = 0000000
# Digit = 1, abcdefg = 0110000
# Digit = 1, abcdefg = 0000000
# Digit = 0, abcdefg = 0000000
# Digit = 1, abcdefg = 0110000
# Digit = 0, abcdefg = 0000000
# Digit = 0, abcdefg = 1111110
# Digit = 1, abcdefg = 0110000
# Digit = 1, abcdefg = 0000000
# Digit = 1, abcdefg = 0110000
# Digit = 0, abcdefg = 0000000
# Digit = 0, abcdefg = 1111110
# Digit = 1, abcdefg = 0110000
# Digit = 0, abcdefg = 0000000
# Digit = 1, abcdefg = 0000000
# Digit = 0, abcdefg = 1111110
# Digit = 1, abcdefg = 0000000
```

 

0 1 2 3 4 5 6 7
8 9 A B C D E F

7-segment decoder

