



# **Verilog HDL**

## **Assignment 6**

### **FSM**

By: Magdy Ahmed Abbas Abdelhamid

# Question 1

## SEQUENCE\_010\_MOORE

### Verilog Code:

```
module Sequence_010_Moore (x, clk, rst, y, count);
parameter STORE = 2'b00;
parameter IDLE = 2'b01;
parameter ZERO = 2'b10;
parameter ONE = 2'b11;
input x, clk, rst;
output reg y;
output reg [9:0] count;
reg [1:0] cs, ns;
// Next state Logic
always @(cs or x) begin
    case (cs)
        STORE :
            if (x)
                ns = IDLE;
            else
                ns = ZERO;
        IDLE :
            if (x)
                ns = IDLE;
            else
                ns = ZERO;
        ZERO :
            if (x)
                ns = ONE;
            else
                ns = ZERO;
        ONE :
            if (x)
                ns = IDLE;
            else
                ns = STORE;
        default : ns = IDLE;
    endcase
end
```

```

// State Memory
always @(posedge clk or posedge rst) begin
    if (rst) begin
        cs <= IDLE;
        count <= 0;
    end
    else
        cs <= ns;
end

// Output Logic
always @(cs) begin
    case (cs)
        STORE : begin
            y = 1;
            count = count + 1;
        end
        IDLE,ZERO,ONE : y = 0;
    endcase
end

endmodule

```

## Testbench Code:

```
module Sequence_010_Moore_tb ();

parameter STORE = 2'b00;
parameter IDLE = 2'b01;
parameter ZERO = 2'b10;
parameter ONE = 2'b11;

reg x, clk, rst;
wire y;
wire [9:0] count;

Sequence_010_Moore #(STORE, IDLE, ZERO, ONE) s1(x, clk, rst, y, count);

initial begin
    clk = 0;
    forever
        #25 clk = ~clk;
end

initial begin
    rst = 1;
    #50;
    rst = 0;
    x = 0;
    #50;
    x = 1;
    #50;
    x = 0;
    #50;

    if ((y != 1) && (count != 1)) begin
        $display("The FSM Design is Wrong! ");
        $stop;
    end

    repeat (50) begin
        @(negedge clk);
        x = $random;
    end
    #2 $stop;
end


initial
    $monitor("time = %0t, x = %b, clk = %b, rst = %b, y = %b, count = %b", $time, x, clk, rst, y, count);

endmodule
```


## Do File for (Sequence\_010\_Moore) Question 1

```
vlib work
vlog Sequence_010_Moore.v Sequence_010_Moore_tb.v
vsim -voptargs = +acc work.Sequence_010_Moore_tb
add wave *
run -all
```

**Waveform:**

 

Name	Type	Size	Description
x	Input	1 bit	Input sequence
clk			Clock
rst			Active high asynchronous reset
y	Output	1 bit	Output that is HIGH when the sequence 010 is detected
count		10 bits	Outputs the number of time the pattern was detected

 


```


# time = 1100, x = 1, clk = 0, rst = 0, y = 0, count = 0000000010
# time = 1125, x = 1, clk = 1, rst = 0, y = 0, count = 0000000010
# time = 1150, x = 1, clk = 0, rst = 0, y = 0, count = 0000000010
# time = 1175, x = 1, clk = 1, rst = 0, y = 0, count = 0000000010
# time = 1200, x = 0, clk = 0, rst = 0, y = 0, count = 0000000010
# time = 1225, x = 0, clk = 1, rst = 0, y = 0, count = 0000000010
# time = 1250, x = 1, clk = 0, rst = 0, y = 0, count = 0000000010
# time = 1275, x = 1, clk = 1, rst = 0, y = 0, count = 0000000010
# time = 1300, x = 0, clk = 0, rst = 0, y = 0, count = 0000000010
# time = 1325, x = 0, clk = 1, rst = 0, y = 1, count = 0000000011
# time = 1350, x = 0, clk = 0, rst = 0, y = 1, count = 0000000011
# time = 1375, x = 0, clk = 1, rst = 0, y = 0, count = 0000000011
# time = 1400, x = 0, clk = 0, rst = 0, y = 0, count = 0000000011
# time = 1425, x = 0, clk = 1, rst = 0, y = 0, count = 0000000011
# time = 1450, x = 1, clk = 0, rst = 0, y = 0, count = 0000000011
# time = 1475, x = 1, clk = 1, rst = 0, y = 0, count = 0000000011
# time = 1500, x = 0, clk = 0, rst = 0, y = 0, count = 0000000011
# time = 1525, x = 0, clk = 1, rst = 0, y = 1, count = 0000000100
# time = 1550, x = 1, clk = 0, rst = 0, y = 1, count = 0000000100
# time = 1575, x = 1, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1600, x = 1, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1625, x = 1, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1650, x = 1, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1675, x = 1, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1700, x = 1, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1725, x = 1, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1750, x = 0, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1775, x = 0, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1800, x = 0, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1825, x = 0, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1850, x = 0, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1875, x = 0, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1900, x = 0, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1925, x = 0, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 1950, x = 1, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 1975, x = 1, clk = 1, rst = 0, y = 0, count = 0000000100
# time = 2000, x = 0, clk = 0, rst = 0, y = 0, count = 0000000100
# time = 2025, x = 0, clk = 1, rst = 0, y = 1, count = 0000000101
# time = 2050, x = 1, clk = 0, rst = 0, y = 1, count = 0000000101
# time = 2075, x = 1, clk = 1, rst = 0, y = 0, count = 0000000101
# time = 2100, x = 1, clk = 0, rst = 0, y = 0, count = 0000000101
# time = 2125, x = 1, clk = 1, rst = 0, y = 0, count = 0000000101
# time = 2150, x = 1, clk = 0, rst = 0, y = 0, count = 0000000101
# time = 2175, x = 1, clk = 1, rst = 0, y = 0, count = 0000000101
# time = 2200, x = 1, clk = 0, rst = 0, y = 0, count = 0000000101
# time = 2225, x = 1, clk = 1, rst = 0, y = 0, count = 0000000101
# time = 2250, x = 1, clk = 0, rst = 0, y = 0, count = 0000000101
# time = 2275, x = 1, clk = 1, rst = 0, y = 0, count = 0000000101
# time = 2300, x = 0, clk = 0, rst = 0, y = 0, count = 0000000101

```

## Schematic after the Elaboration:

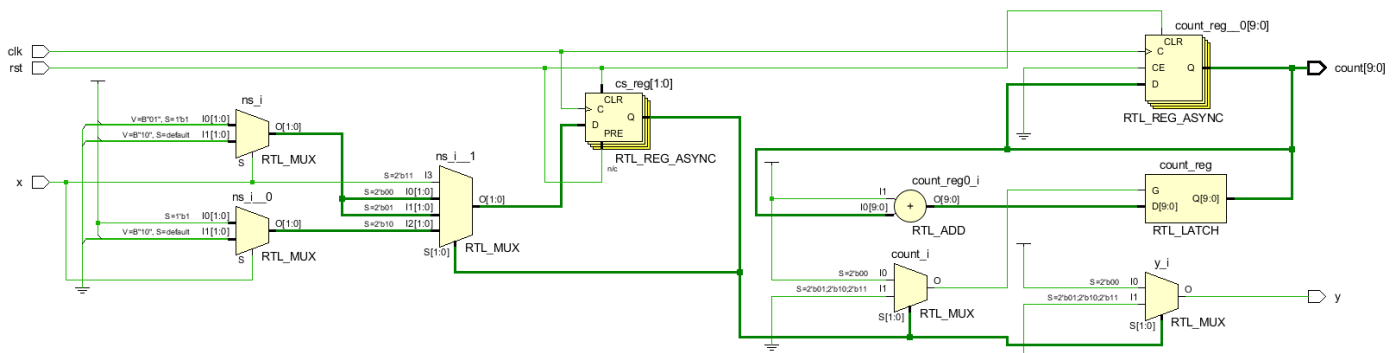


## Schematic after the Synthesis:

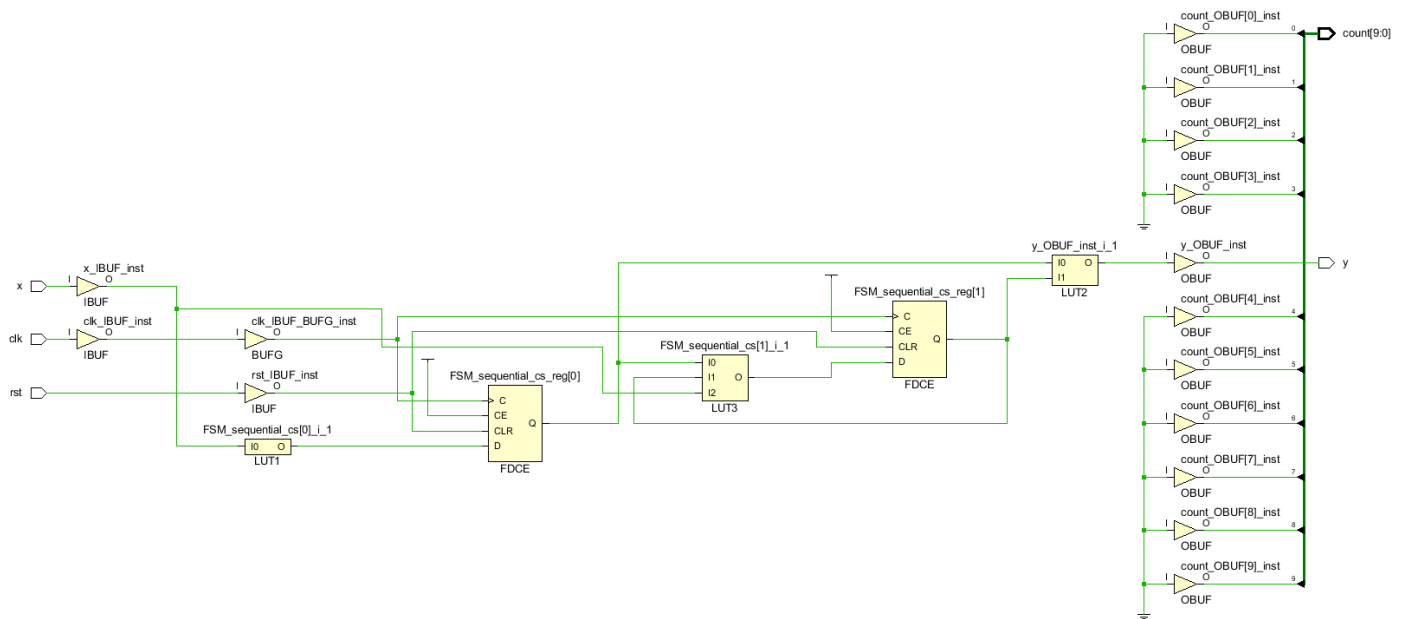


## Utilization Report:

### Summary

Resource	Utilization	Available	Utilization %
LUT	3	20800	0.01
FF	2	41600	0.00
IO	14	106	13.21

 

## Device after implementation:

 



## Question 2



### TESLA - CAR

#### Verilog Code:

```
module Tesla_Car (speed_limit, car_speed, leading_distance, clk, rst, unlock_doors, accel

parameter MIN_DISTANCE = 7'd40; // 40 meters
parameter ACCELERATE = 2'b00;
parameter STOP = 2'b01;
parameter DECELERATE = 2'b10;
input [7:0] speed_limit, car_speed;
input [6:0] leading_distance;
input clk, rst;
output reg unlock_doors, accelerate_car;
reg [1:0] ns, cs;
// Next State Logic
always @(*) begin
    case (cs)
        ACCELERATE :
            if ((leading_distance >= MIN_DISTANCE) && (car_speed < speed_limit))
                ns = ACCELERATE;
            else if ((leading_distance < MIN_DISTANCE) || (car_speed > speed_limit))
                ns = DECELERATE;
        STOP :
            if (leading_distance < MIN_DISTANCE)
                ns = STOP;
            else if (leading_distance >= MIN_DISTANCE)
                ns = ACCELERATE;
        DECELERATE :
            if ((leading_distance < MIN_DISTANCE) || (car_speed > speed_limit))
                ns = DECELERATE;
            else if ((leading_distance >= MIN_DISTANCE) && (car_speed
                < speed_limit))
                ns = ACCELERATE;
            else if (car_speed == 0)
                ns = STOP;
        default : ns = STOP;
    endcase
end
```

```

// State Memory
always @(posedge clk or posedge rst) begin
    if (rst)
        cs <= STOP;
    else
        cs <= ns;
end

// Output Logic
always @(cs) begin
    case (cs)
        ACCELERATE : begin
            unlock_doors = 0;
            accelerate_car = 1;
        end
        STOP : begin
            unlock_doors = 1;
            accelerate_car = 0;
        end
        DECELERATE : begin
            unlock_doors = 0;
            accelerate_car = 0;
        end
    endcase
end

endmodule

```

## Testbench Code:

```
module Tesla_Car_tb ();
parameter MIN_DISTANCE = 7'd40; // 40 meters
parameter ACCELERATE = 2'b00;
parameter STOP = 2'b01;
parameter DECELERATE = 2'b10;
reg [7:0] speed_limit, car_speed;
reg [6:0] leading_distance;
reg clk, rst;
wire unlock_doors, accelerate_car;
Tesla_Car #(MIN_DISTANCE, ACCELERATE, STOP, DECELERATE)
T1(speed_limit, car_speed, leading_distance, clk, rst, unlock_doors, accelerate_car);

initial begin
    clk = 0;
    forever
        #25 clk = ~clk;
end
initial begin
    rst = 1;
    speed_limit = 8'd80;
    leading_distance = 7'd50;
    car_speed = 0;
    #100;
    // Test Acceleration and Deceleration With Speed Limit
    car_speed = 8'd20;
    rst = 0;
    #1000;
    // Test the Safety For Car Crashes with Leading Vehicle / Object
    leading_distance = 7'd10;
    #1000;
    $stop;
end
// Change Speed of the Car During the Current State
always @(negedge clk) begin
    if (~rst) begin
        if (unlock_doors == 0) begin
            if (accelerate_car)
                car_speed = car_speed + 1;
            else
                car_speed = car_speed - 1;
        end
    end
end
initial
$monitor ("clk = %b, rst = %b, speed_limit = %d m/sec, car_speed = %d m/sec, leading_distance
          = %d m, unlock_doors = %b, accelerate_car = %b"
          , clk, rst, speed_limit, car_speed, leading_distance, unlock_doors, accelerate_car);
endmodule
```

## Do File for (Tesla\_Car) Question 2

```
vlib work
vlog Tesla_Car.v Tesla_Car_tb.v
vsim -voptargs = +acc work.Tesla_Car_tb
add wave *
run -all
```

### Waveform:




Name	Type	Size	Description
speed_limit	Input	8 bits	Allowable speed limit of the highway
car_speed		8 bits	Current car speed
leading_distance		7 bits	Distance between the car and the vehicle/object in front of it
clk		1 bit	Clock
rst	Output	1 bit	Active high asynchronous reset
unlock_doors		1 bit	Signal that unlock the car doors when HIGH
accelerate_car		1 bit	Signal that control the flow of the fuel to the engine to accelerate the car when HIGH



### Schematic after the Elaboration:




# Schematic after the Synthesis:

 


# Utilization Report:

## Summary

Resource	Utilization	Available	Utilization %
LUT	17	20800	0.08
FF	8	41600	0.02
IO	24	106	22.64

 

## Device after implementation:

 

## Question 3

### GRAY CODE MOORE FSM

#### Verilog Code:

```
module Gray_Code_Moore (clk, rst, y);

parameter A = 2'b00;
parameter B = 2'b01;
parameter C = 2'b10;
parameter D = 2'b11;

input clk, rst;
output reg [1:0] y;

reg [1:0] cs, ns;

// Next State Logic
always @(cs) begin
    case (cs)
        A : ns = B;
        B : ns = C;
        C : ns = D;
        D : ns = A;
    endcase
end

// State Memory
always @(posedge clk or posedge rst) begin
    if (rst)
        cs <= A;
    else
        cs <= ns;
end

// Output Logic
always @(cs) begin
    case (cs)
        A : y = 2'b00;
        B : y = 2'b01;
        C : y = 2'b11;
        D : y = 2'b10;
    endcase
end
endmodule
```



```
module Gray_Code_Ref (clk, rst, gray_out);

input clk, rst;
output [1:0] gray_out;

reg [1:0] binary_cnt;

always @(posedge clk or posedge rst) begin
    if (rst)
        binary_cnt <= 0;
    else begin
        binary_cnt <= binary_cnt + 1;
    end
end

assign gray_out[1] = binary_cnt[1];
assign gray_out[0] = ^binary_cnt;

endmodule
```

## Testbench Code:

```
module Gray_Code_Moore_tb ();

parameter A = 2'b00;
parameter B = 2'b01;
parameter C = 2'b10;
parameter D = 2'b11;

reg clk, rst;
wire [1:0] y_DUT;
wire [1:0] y_REF;

Gray_Code_Moore #(A, B, C, D) DUT (clk, rst, y_DUT);
Gray_Code_Ref REF (clk, rst, y_REF);

initial begin
    clk = 0;
    forever
        #25 clk = ~clk;
end

initial begin
    rst = 1;
    repeat (4) @(negedge clk);
    rst = 0;
    repeat (100) begin
        @(negedge clk);
        if (y_DUT != y_REF) begin
            $display("The FSM Design is Wrong!");
            $stop;
        end
    end
    $stop;
end



initial
    $monitor("time = %0t, CLK = %b, RST = %b, Gray_out = %b",
            $time, clk, rst, y_DUT);

endmodule
```


## Do File for (Gray\_Code\_Moore) Question 3

```
vlib work
vlog Gray_Code_Moore.v Gray_Code_Ref.v Gray_Code_Moore_tb.v
vsim -voptargs = +acc work.Gray_Code_Moore_tb
add wave *
run -all
```

### Waveform:

  

```
# time = 100, CLK = 0, RST = 1, Gray_out = 00
# time = 125, CLK = 1, RST = 1, Gray_out = 00
# time = 150, CLK = 0, RST = 1, Gray_out = 00
# time = 175, CLK = 1, RST = 1, Gray_out = 00
# time = 200, CLK = 0, RST = 0, Gray_out = 00
# time = 225, CLK = 1, RST = 0, Gray_out = 01
# time = 250, CLK = 0, RST = 0, Gray_out = 01
# time = 275, CLK = 1, RST = 0, Gray_out = 11
# time = 300, CLK = 0, RST = 0, Gray_out = 11
# time = 325, CLK = 1, RST = 0, Gray_out = 10
# time = 350, CLK = 0, RST = 0, Gray_out = 10
# time = 375, CLK = 1, RST = 0, Gray_out = 00
# time = 400, CLK = 0, RST = 0, Gray_out = 00
# time = 425, CLK = 1, RST = 0, Gray_out = 01
# time = 450, CLK = 0, RST = 0, Gray_out = 01
# time = 475, CLK = 1, RST = 0, Gray_out = 11
# time = 500, CLK = 0, RST = 0, Gray_out = 11
# time = 525, CLK = 1, RST = 0, Gray_out = 10
# time = 550, CLK = 0, RST = 0, Gray_out = 10
# time = 575, CLK = 1, RST = 0, Gray_out = 00
# time = 600, CLK = 0, RST = 0, Gray_out = 00
# time = 625, CLK = 1, RST = 0, Gray_out = 01
# time = 650, CLK = 0, RST = 0, Gray_out = 01
# time = 675, CLK = 1, RST = 0, Gray_out = 11
# time = 700, CLK = 0, RST = 0, Gray_out = 11
# time = 725, CLK = 1, RST = 0, Gray_out = 10
# time = 750, CLK = 0, RST = 0, Gray_out = 10
# time = 775, CLK = 1, RST = 0, Gray_out = 00
# time = 800, CLK = 0, RST = 0, Gray_out = 00
# time = 825, CLK = 1, RST = 0, Gray_out = 01
# time = 850, CLK = 0, RST = 0, Gray_out = 01
# time = 875, CLK = 1, RST = 0, Gray_out = 11
# time = 900, CLK = 0, RST = 0, Gray_out = 11
# time = 925, CLK = 1, RST = 0, Gray_out = 10
# time = 950, CLK = 0, RST = 0, Gray_out = 10
# time = 975, CLK = 1, RST = 0, Gray_out = 00
# time = 1000, CLK = 0, RST = 0, Gray_out = 00
```

 

## Constraint File:

```
## Clock signal
set_property -dict { PACKAGE_PIN W5  IOSTANDARD LVCMOS33 } [get_ports clk]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]


## LEDs
set_property -dict { PACKAGE_PIN U16  IOSTANDARD LVCMOS33 } [get_ports {y[0]}]
set_property -dict { PACKAGE_PIN E19  IOSTANDARD LVCMOS33 } [get_ports {y[1]}]

##Buttons
set_property -dict { PACKAGE_PIN U18  IOSTANDARD LVCMOS33 } [get_ports rst]


## Configuration options, can be used for all designs
set_property CONFIG_VOLTAGE 3.3 [current_design]
set_property CFGBVS VCCO [current_design]

## SPI configuration mode options for QSPI boot, can be used for all designs
set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
set_property CONFIG_MODE SPIx4 [current_design]
```

## Schematic after the Elaboration:

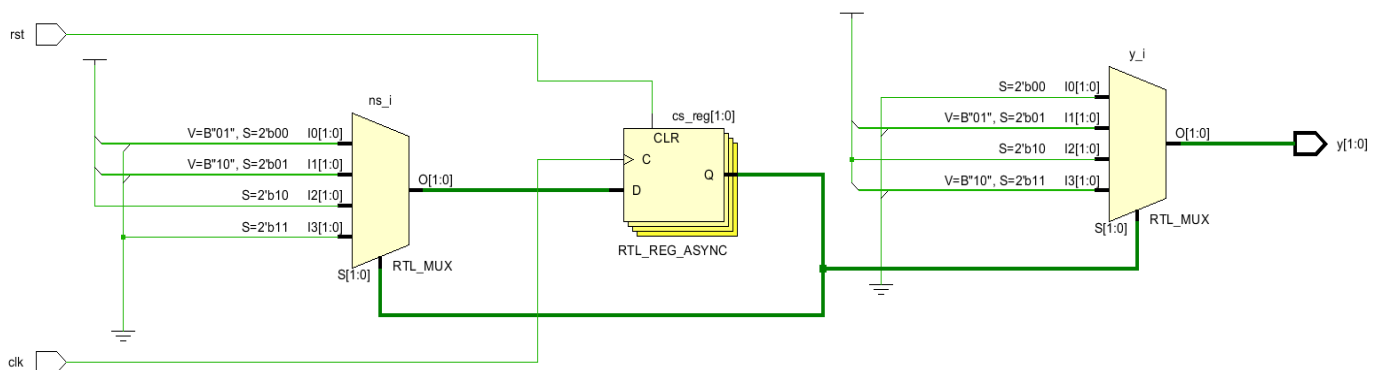


## Schematic after the Synthesis:

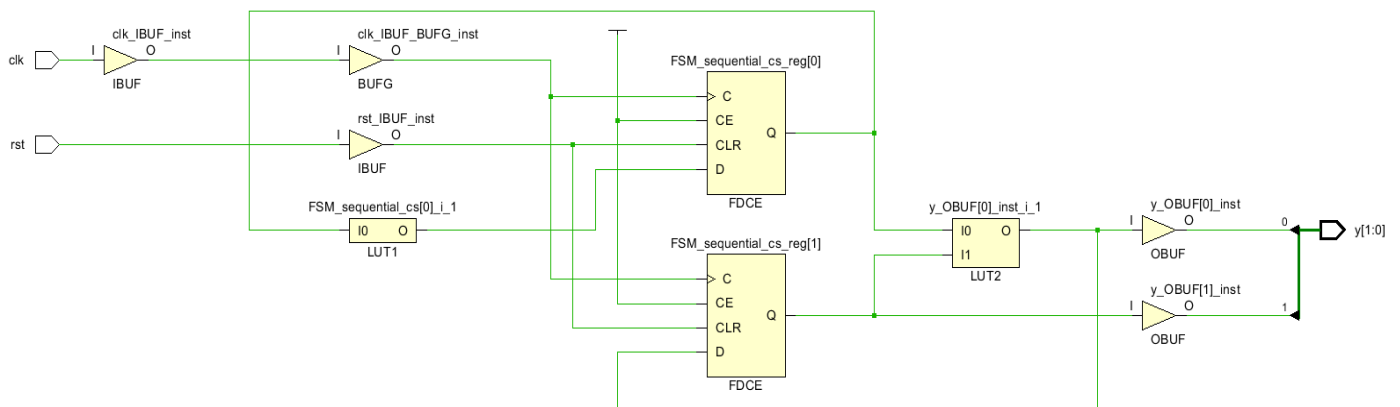


# Utilization Report:

## Summary


Resource	Utilization	Available	Utilization %
LUT	2	20800	0.01
FF	2	41600	0.00
IO	4	106	3.77

 

# Device after implementation:

 

## Successful Bitstream Generation:

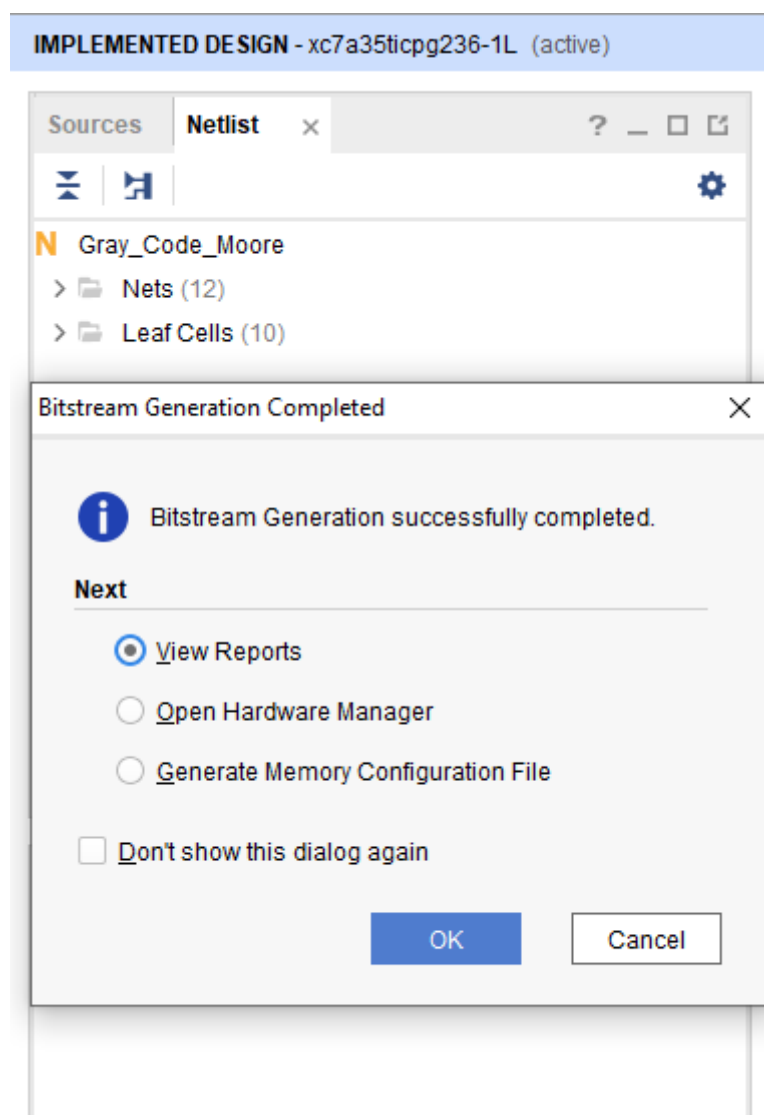


### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

<b>Total On-Chip Power:</b>	<b>0.068 W</b>
<b>Design Power Budget:</b>	<b>Not Specified</b>
<b>Power Budget Margin:</b>	<b>N/A</b>
<b>Junction Temperature:</b>	<b>25.3°C</b>
<b>Thermal Margin:</b>	<b>74.7°C (14.9 W)</b>
<b>Effective <math>\theta_{JA}</math>:</b>	<b>5.0°C/W</b>
<b>Power supplied to off-chip devices:</b>	<b>0 W</b>
<b>Confidence level:</b>	<b>Medium</b>

[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

## Question 4

### SEQUENCE DETECTOR MEALY

#### Verilog Code:

```
module Sequence_Mealy (clk,rst,in,y);
parameter S0 = 2'b00;
parameter S1 = 2'b01;
parameter S2 = 2'b10;
parameter S3 = 2'b11;
input clk,rst,in;
output reg y;
reg [1:0] cs,ns;      // Next State Logic
always @(*) begin
    case (cs)
        S0 : if (in)
            ns = S1;
            else
            ns = S0;
        S1 : if (in)
            ns = S2;
            else
            ns = S1;
        S2 : if (in)
            ns = S3;
            else
            ns = S2;
        S3 : if (in)
            ns = S1;
            else
            ns = S0;
    endcase
end // Memory State
always @(posedge clk or posedge rst) begin
    if (rst)
        cs <= S0;
    else
        cs <= ns;
end // Output Logic
always @(*) begin
    if ((cs == S2) && (in == 1))
        y = 1;
    else
        y = 0;
end endmodule
```

## Testbench Code:

```
module Sequence_Mealy_tb ();

parameter S0 = 2'b00;
parameter S1 = 2'b01;
parameter S2 = 2'b10;
parameter S3 = 2'b11;

reg clk, rst, in;
wire y;

Sequence_Mealy #(S0,S1,S2,S3) DUT(clk, rst, in, y);

integer counter = 0;

initial begin
    clk = 0;
    forever
        #25 clk = ~clk;
end

initial begin
    rst = 1; in = 0;
    repeat (2) @(negedge clk); // Delay for 2 Clock Cycles
    rst = 0;
    repeat (100) begin
        @(negedge clk);
        in = $random;
        if (in == 1)
            counter = counter + 1;
    end
    $stop;
end

always @(y) begin
    if (y) begin
        if ((counter % 3 == 0 && y != 1) || (counter % 3 != 0 && y == 0)) begin
            $display("The FSM Design is Wrong!");
            $stop;
        end
    end
end

initial
    $monitor("time = %0t, clk = %b, rst = %b, in = %b, y = %b, Counter = %b",
            $time, clk, rst, in, y, counter);




endmodule
```



## Do File for (Sequence\_Mealy) Question 4

```
vlib work
vlog Sequence_Mealy.v Sequence_Mealy_tb.v
vsim -voptargs = +acc work.Sequence_Mealy_tb
add wave *
run -all
```


### Waveform:

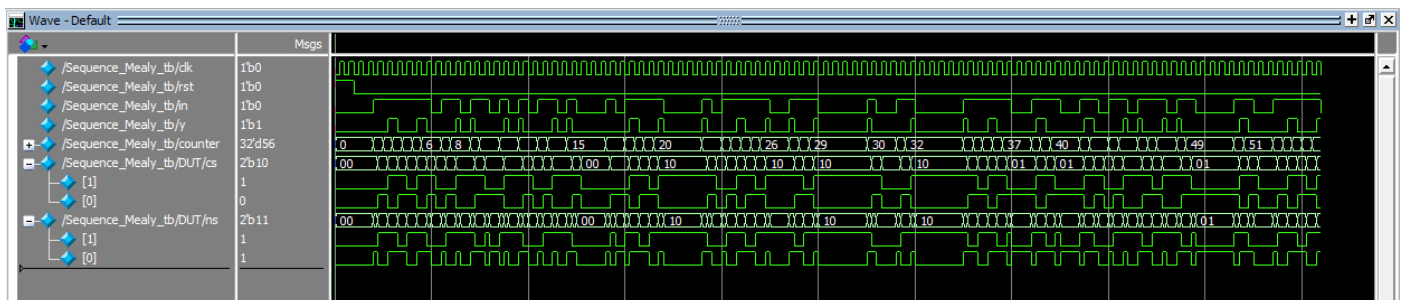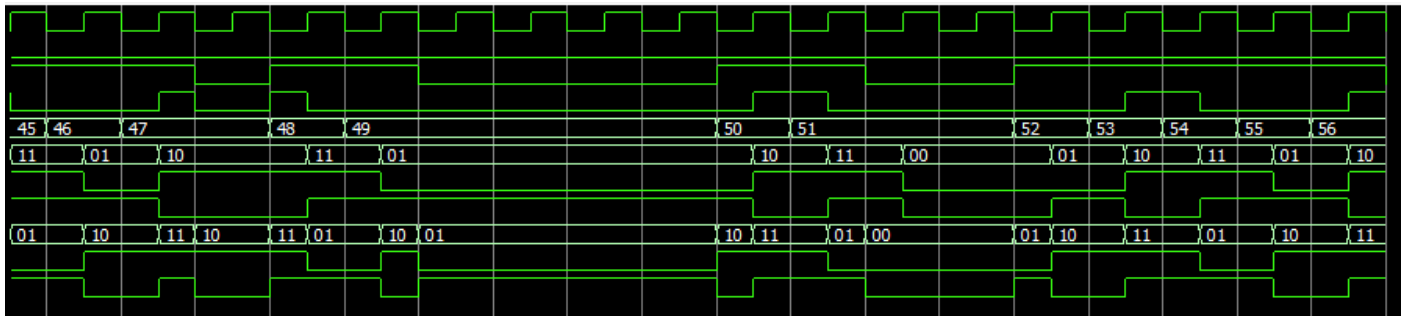 

```

# time = 100, clk = 0, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000000
# time = 125, clk = 1, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000000
# time = 150, clk = 0, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000000
# time = 175, clk = 1, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000000
# time = 200, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000001
# time = 225, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000001
# time = 250, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000010
# time = 275, clk = 1, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000010
# time = 300, clk = 0, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000011
# time = 325, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000011
# time = 350, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000100
# time = 375, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000100
# time = 400, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000101
# time = 425, clk = 1, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000101
# time = 450, clk = 0, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000110
# time = 475, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000110
# time = 500, clk = 0, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000110
# time = 525, clk = 1, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000110
# time = 550, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000111
# time = 575, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000111
# time = 600, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000100
# time = 625, clk = 1, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000100
# time = 650, clk = 0, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000100
# time = 675, clk = 1, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000100
# time = 700, clk = 0, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000101
# time = 725, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000101
# time = 750, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000101
# time = 775, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000101
# time = 800, clk = 0, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000101
# time = 825, clk = 1, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000101
# time = 850, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000101
# time = 875, clk = 1, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000101
# time = 900, clk = 0, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000101
# time = 925, clk = 1, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000101
# time = 950, clk = 0, rst = 0, in = 1, y = 1, Counter = 00000000000000000000000000000110
# time = 975, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000110
# time = 1000, clk = 0, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000110
# time = 1025, clk = 1, rst = 0, in = 0, y = 0, Counter = 00000000000000000000000000000110
# time = 1050, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000101
# time = 1075, clk = 1, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000101
# time = 1100, clk = 0, rst = 0, in = 1, y = 0, Counter = 00000000000000000000000000000110

```

 

## Constraint File:

```
## Clock signal
set_property -dict { PACKAGE_PIN W5  IOSTANDARD LVCMOS33 } [get_ports clk]
create_clock -add -name sys_clk_pin -period 10.00 -waveform {0 5} [get_ports clk]

## Switches
set_property -dict { PACKAGE_PIN V17  IOSTANDARD LVCMOS33 } [get_ports {in}]


## LEDs
set_property -dict { PACKAGE_PIN U16  IOSTANDARD LVCMOS33 } [get_ports {y}]

##Buttons
set_property -dict { PACKAGE_PIN U18  IOSTANDARD LVCMOS33 } [get_ports rst]


## Configuration options, can be used for all designs
set_property CONFIG_VOLTAGE 3.3 [current_design]
set_property CFGBVS VCCO [current_design]

## SPI configuration mode options for QSPI boot, can be used for all designs
set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
set_property CONFIG_MODE SPIx4 [current_design]
```

## Schematic after the Elaboration:

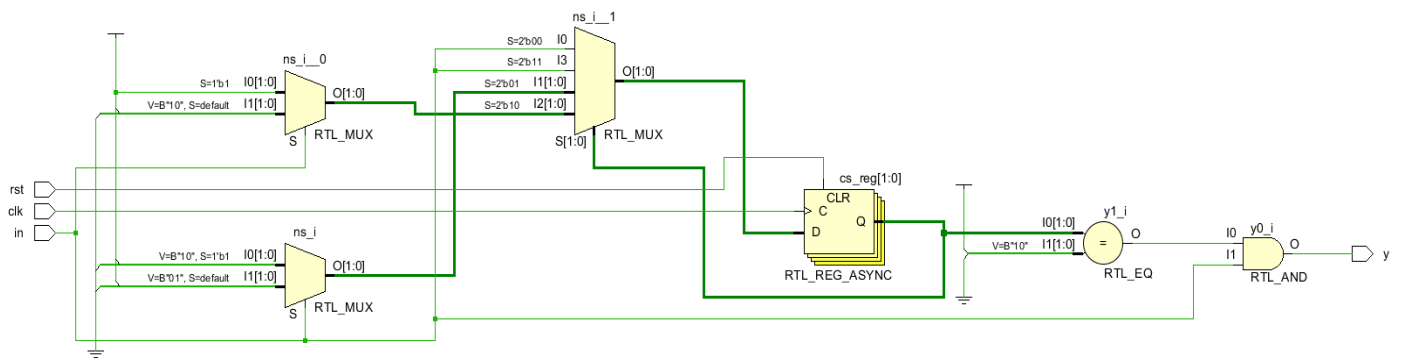


## Schematic after the Synthesis:

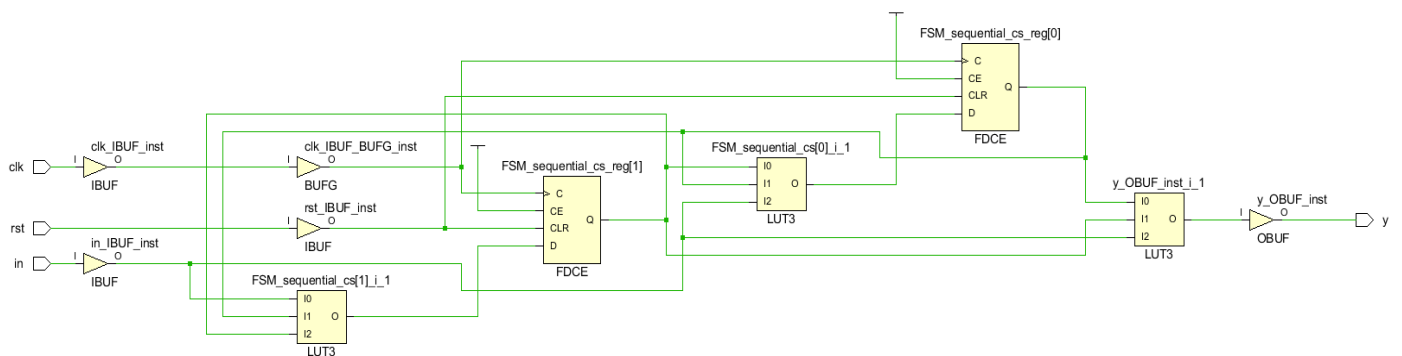


# Utilization Report:

## Summary


Resource	Utilization	Available	Utilization %
LUT	3	20800	0.01
FF	2	41600	0.00
IO	4	106	3.77

 

# Device after implementation:

 

## Successful Bitstream Generation:

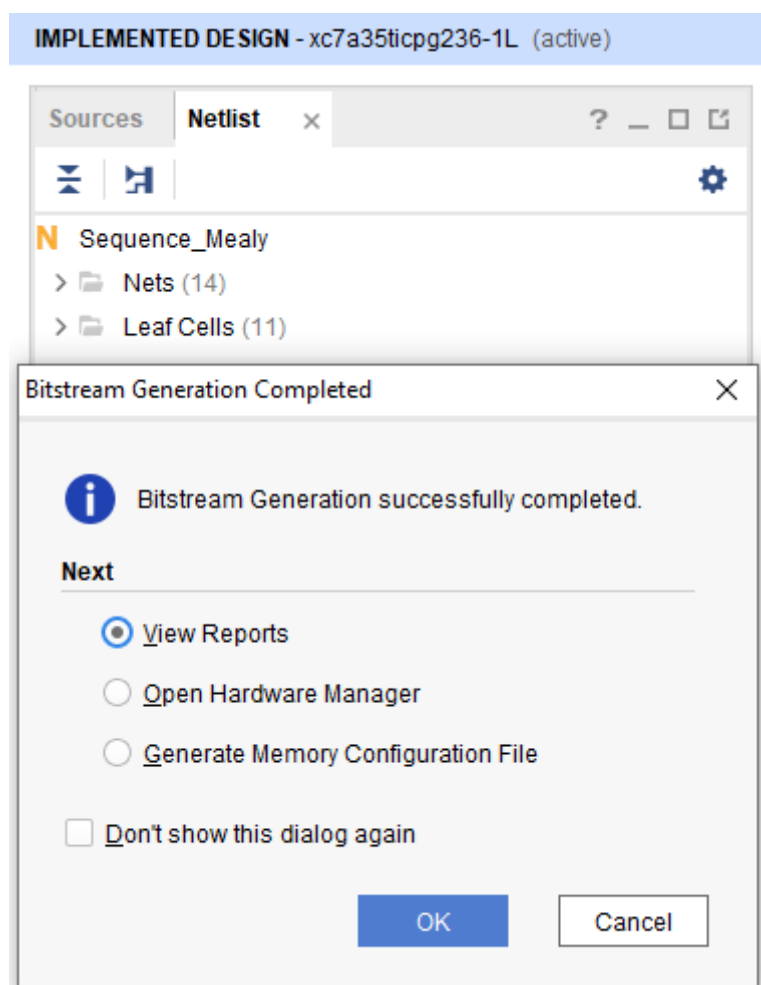


### Summary

Power analysis from Implemented netlist. Activity derived from constraints files, simulation files or vectorless analysis.

**Total On-Chip Power:** 0.063 W  
**Design Power Budget:** Not Specified  
**Power Budget Margin:** N/A  
**Junction Temperature:** 25.3°C  
**Thermal Margin:** 74.7°C (14.9 W)  
**Effective  $\theta_{JA}$ :** 5.0°C/W  
**Power supplied to off-chip devices:** 0 W  
**Confidence level:** Medium  
[Launch Power Constraint Advisor](#) to find and fix invalid switching activity

### On-Chip Power

 

## Question 5

### ALSU

#### Verilog Code:

```
module ALSU (A,B, opcode, cin, serial_in, direction, red_op_A, red_op_B, bypass_A, bypass_B, clk, rst, out, leds);

parameter INPUT_PRIORITY = "A";
parameter FULL_ADDER = "ON";
input clk, rst, cin, serial_in, red_op_A, red_op_B, bypass_A, bypass_B, direction;
input [2:0] A,B, opcode;
output reg [15:0] leds;
output reg [5:0] out;
reg [2:0] A_FF, B_FF, opcode_FF;
reg cin_FF, serial_in_FF, red_op_A_FF, red_op_B_FF, bypass_A_FF, bypass_B_FF, direction_FF;
wire invalid_red_op, invalid_opcode, invalid;
assign invalid_red_op = (red_op_A_FF | red_op_B_FF) & (opcode_FF[1] | opcode_FF[2]);
assign invalid_opcode = opcode_FF[1] & opcode_FF[2];
assign invalid = invalid_red_op | invalid_opcode;
wire [5:0] multi_out;
wire [3:0] adder_out;

generate
  if (FULL_ADDER == "ON")
    c_addsub_0 Adder (
      .A(A_FF),    // input wire [2 : 0] A
      .B(B_FF),    // input wire [2 : 0] B
      .C_IN(cin_FF), // input wire C_IN
      .S(adder_out) // output wire [3 : 0] S
    );
  else if (FULL_ADDER == "OFF")
    c_addsub_0 Adder (
      .A(A_FF),    // input wire [2 : 0] A
      .B(B_FF),    // input wire [2 : 0] B
      .C_IN(0), // input wire C_IN
      .S(adder_out) // output wire [3 : 0] S
    );
endgenerate

mult_gen_0 Multiplier (
  .A(A_FF), // input wire [2 : 0] A
  .B(B_FF), // input wire [2 : 0] B
  .P(multi_out) // output wire [5 : 0] P
);
```

```


always @(posedge clk or posedge rst) begin
    if (rst) begin
        A_FF <= 0; B_FF <= 0; opcode_FF <= 0; cin_FF <= 0; serial_in_FF <= 0; red_op_A_FF <= 0;
        red_op_B_FF <= 0; bypass_A_FF <= 0; bypass_B_FF <= 0; direction_FF <= 0;
    end begin
        A_FF <= A; B_FF <= B; opcode_FF <= opcode; cin_FF <= cin; serial_in_FF <= serial_in; red_op_A_FF
            <= red_op_A;
        red_op_B_FF <= red_op_B; bypass_A_FF <= bypass_A; bypass_B_FF <= bypass_B; direction_FF <
            = direction;
    end
end
always @(posedge clk or posedge rst) begin
    if (rst) begin
        leds <= 0;
    end else begin
        if (invalid)
            leds = ~leds;
        leds <= 0;
    end
end
always @(posedge clk or posedge rst) begin
    if (rst) begin
        out <= 0;
    end
    else begin
        if (bypass_A_FF && bypass_B_FF)
            out <= (INPUT_PRIORITY == "A")? A_FF : B_FF;
        else if (bypass_A_FF)
            out <= A_FF;
        else if (bypass_B_FF)
            out <= B_FF;
        else begin
            if (invalid) begin
                out <= 0;
            end else begin
                case (opcode_FF)
                    3'h0 : begin
                        if (red_op_A_FF && red_op_B_FF)
                            out <= (INPUT_PRIORITY == "A")? &A_FF : &B_FF;
                        else if (red_op_A_FF)
                            out <= &A_FF;
                        else if (red_op_B_FF)
                            out <= &B_FF;
                        else
                            out <= A_FF & B_FF;
                    end
                end
            end
        end
    end
end

```

```

3'h1 : begin
  if (red_op_A_FF && red_op_B_FF)
    out <= (INPUT_PRIORITY == "A")? ^A_FF : ^B_FF;
  else if (red_op_A_FF)
    out <= ^A_FF;
  else if (red_op_B_FF)
    out <= ^B_FF;
  else
    out <= A_FF ^ B_FF;
  end
3'h2 : out <= adder_out;
3'h3 : out <= multi_out;
3'h4 : begin
  if (direction_FF)
    out <= {out[4:0],serial_in_FF};
  else
    out <= {serial_in_FF,out[5:1]};
  end
3'h5 : begin
  if (direction_FF)
    out <= {out[4:0],out[5]};
  else
    out <= {out[0],out[5:1]};
  end
endcase
end
end
end
end
endmodule

```

 



## Constraint File:

```
## Clock signal
set_property -dict {PACKAGE_PIN W5 IOSTANDARD LVCMOS33} [get_ports clk]
create_clock -period 10.000 -name sys_clk_pin -waveform {0.000 5.000} -add [get_ports clk]


## Switches
set_property -dict {PACKAGE_PIN V17 IOSTANDARD LVCMOS33} [get_ports {opcode[0]}]
set_property -dict {PACKAGE_PIN V16 IOSTANDARD LVCMOS33} [get_ports {opcode[1]}]
set_property -dict {PACKAGE_PIN W16 IOSTANDARD LVCMOS33} [get_ports {opcode[2]}]
set_property -dict {PACKAGE_PIN W17 IOSTANDARD LVCMOS33} [get_ports {A[0]}]
set_property -dict {PACKAGE_PIN W15 IOSTANDARD LVCMOS33} [get_ports {A[1]}]
set_property -dict {PACKAGE_PIN V15 IOSTANDARD LVCMOS33} [get_ports {A[2]}]
set_property -dict {PACKAGE_PIN W14 IOSTANDARD LVCMOS33} [get_ports {B[0]}]
set_property -dict {PACKAGE_PIN W13 IOSTANDARD LVCMOS33} [get_ports {B[1]}]
set_property -dict {PACKAGE_PIN V2 IOSTANDARD LVCMOS33} [get_ports {B[2]}]
set_property -dict {PACKAGE_PIN T3 IOSTANDARD LVCMOS33} [get_ports cin]
set_property -dict {PACKAGE_PIN T2 IOSTANDARD LVCMOS33} [get_ports red_op_A]
set_property -dict {PACKAGE_PIN R3 IOSTANDARD LVCMOS33} [get_ports red_op_B]
set_property -dict {PACKAGE_PIN W2 IOSTANDARD LVCMOS33} [get_ports bypass_A]
set_property -dict {PACKAGE_PIN U1 IOSTANDARD LVCMOS33} [get_ports bypass_B]
set_property -dict {PACKAGE_PIN T1 IOSTANDARD LVCMOS33} [get_ports direction]
set_property -dict {PACKAGE_PIN R2 IOSTANDARD LVCMOS33} [get_ports serial_in]

## LEDs
set_property -dict {PACKAGE_PIN U16 IOSTANDARD LVCMOS33} [get_ports {leds[0]}]
set_property -dict {PACKAGE_PIN E19 IOSTANDARD LVCMOS33} [get_ports {leds[1]}]
set_property -dict {PACKAGE_PIN U19 IOSTANDARD LVCMOS33} [get_ports {leds[2]}]
set_property -dict {PACKAGE_PIN V19 IOSTANDARD LVCMOS33} [get_ports {leds[3]}]
set_property -dict {PACKAGE_PIN W18 IOSTANDARD LVCMOS33} [get_ports {leds[4]}]
set_property -dict {PACKAGE_PIN U15 IOSTANDARD LVCMOS33} [get_ports {leds[5]}]
set_property -dict {PACKAGE_PIN U14 IOSTANDARD LVCMOS33} [get_ports {leds[6]}]
set_property -dict {PACKAGE_PIN V14 IOSTANDARD LVCMOS33} [get_ports {leds[7]}]
set_property -dict {PACKAGE_PIN V13 IOSTANDARD LVCMOS33} [get_ports {leds[8]}]
set_property -dict {PACKAGE_PIN V3 IOSTANDARD LVCMOS33} [get_ports {leds[9]}]
set_property -dict {PACKAGE_PIN W3 IOSTANDARD LVCMOS33} [get_ports {leds[10]}]
set_property -dict {PACKAGE_PIN U3 IOSTANDARD LVCMOS33} [get_ports {leds[11]}]
set_property -dict {PACKAGE_PIN P3 IOSTANDARD LVCMOS33} [get_ports {leds[12]}]
set_property -dict {PACKAGE_PIN N3 IOSTANDARD LVCMOS33} [get_ports {leds[13]}]
set_property -dict {PACKAGE_PIN P1 IOSTANDARD LVCMOS33} [get_ports {leds[14]}]
set_property -dict {PACKAGE_PIN L1 IOSTANDARD LVCMOS33} [get_ports {leds[15]}]


##Buttons
set_property -dict {PACKAGE_PIN U18 IOSTANDARD LVCMOS33} [get_ports rst]

## Configuration options, can be used for all designs
set_property CONFIG_VOLTAGE 3.3 [current_design]
set_property CFGBVS VCCO [current_design]

 
## SPI configuration mode options for QSPI boot, can be used for all designs
set_property BITSTREAM.GENERAL.COMPRESS TRUE [current_design]
set_property BITSTREAM.CONFIG.CONFIGRATE 33 [current_design]
set_property CONFIG_MODE SPIx4 [current_design]
```



## Schematic after the Elaboration:

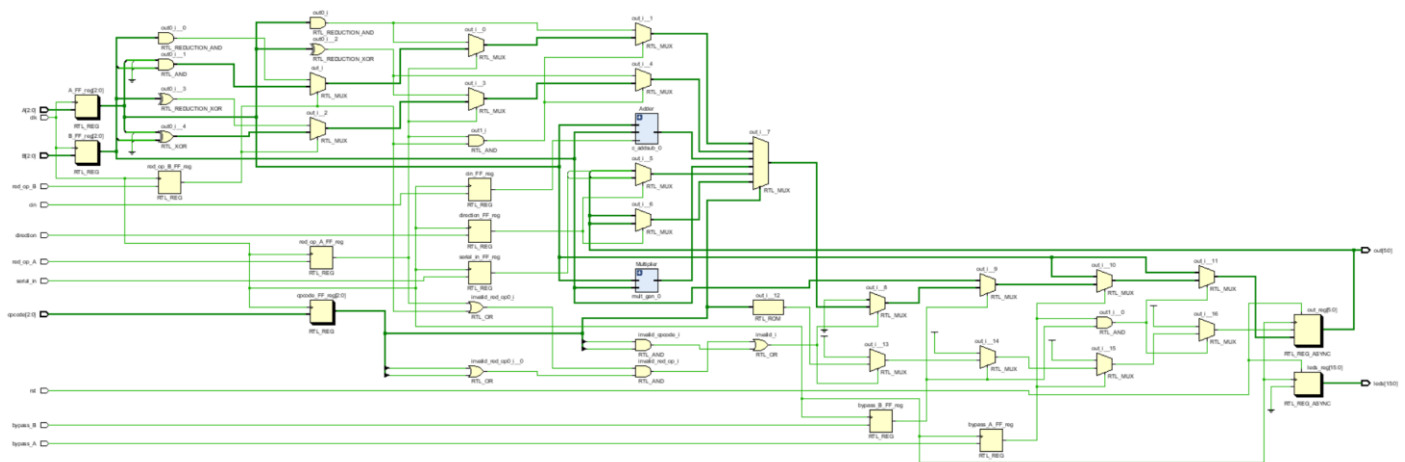


## Schematic after the Synthesis:

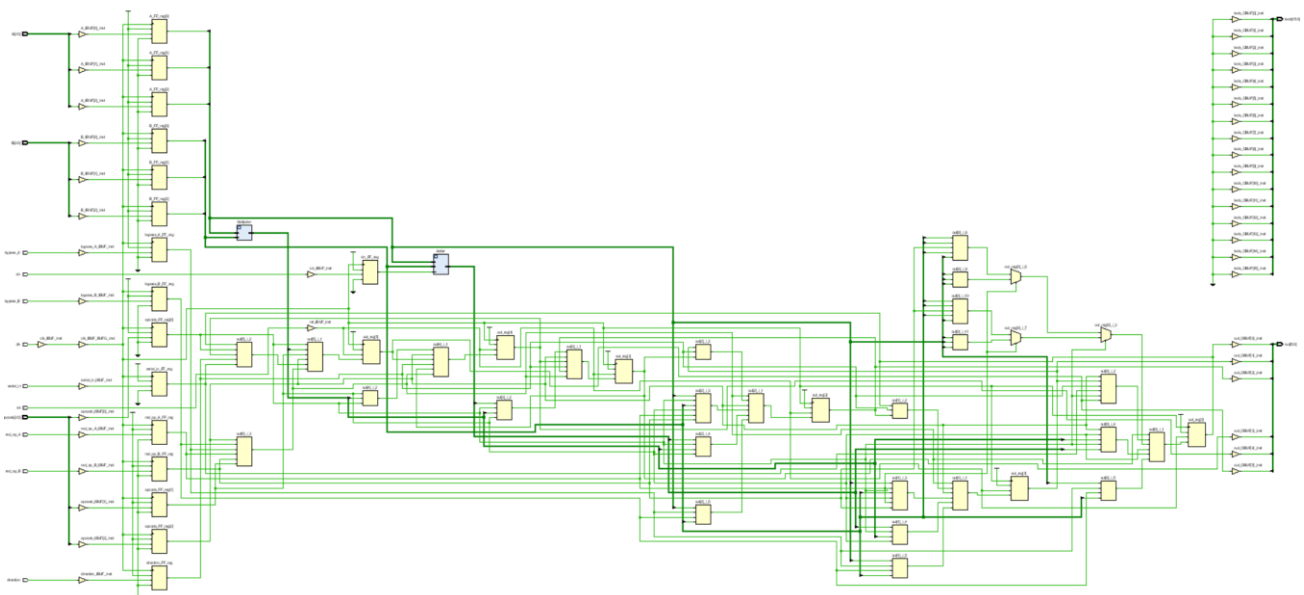


# Utilization Report:

## Summary

Resource	Utilization	Available	Utilization %
LUT	37	20800	0.18
FF	22	41600	0.05
IO	40	106	37.74

 

## Device after implementation:

 

## Successful Bitstream Generation:

