 


Combinational Circuit Design

Design the following circuits with Verilog using assign statements.

1)

- The design has 7 inputs and 2 outputs
- Use assign statements to design the following




2) Implement 4-bit adder using addition operator

- The design takes 2 inputs (A, B) and the summation is assigned to output (C) ignoring the carry

 3) Implement 4-bit adder below using the bitwise operators

- The design takes 3 inputs (A, B, Cin) and 2 outputs (S, Cout)



4) Implement 2-to-4 Decoder using conditional operator (A logic decoder has n input lines and 2^n output lines. Each output line corresponds to a unique combination of the input values.)

- The design has input **A** (2 bits) and output **D** (4 bits)

A_1	A_0	D_3	D_2	D_1	D_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0

5) Implement an even parity generator module. In case you don't know what a parity bit is, please check this [link](#). The design input is a bus where a reduction operator will be used to generate the even parity bit.

- The design has 1 input **A** (8 bits) and 1 output **out_with_parity** (9 bit) where the parity bit calculated will be inserted in the least significant bit of the output bus and the remaining bits will be the input A.
- Use Concatenation

6) Implement a comparator that compares 2 inputs (**A**, **B**) and has 3 outputs using conditional operator.

- The first output **A_greaterthan_B** is high only when A is greater than B
- The second output **A_equals_B** is high only when A equals B
- The third output **A_lessthan_B** is high only when A is less than B



Inputs A and B are 4-bit bus while the 3 outputs are single bits.

Deliverables: The assignment should be submitted as a PDF file with this format <your_name>_Assignment1 for example Kareem_Waseem_Assignment1

Note that your document should be organized as 6 sections corresponding to each design above, and in each section, I am expecting the Verilog code.