



Verilog HDL

Assignment 4 Extended

By: Magdy Ahmed Abbas Abdelhamid

Question 1


HAND - DRAWN SCHEMATIC

1

```
module reg_blocking1(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

 
always @(posedge clk) begin
    if (rst) begin
        q1 = 0;
        q2 = 0;
        out = 0;
    end
    else begin
        q1 = in;
        q2 = q1;
        out = q2;
    end
end
endmodule
```



```
module reg_non_blocking1(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

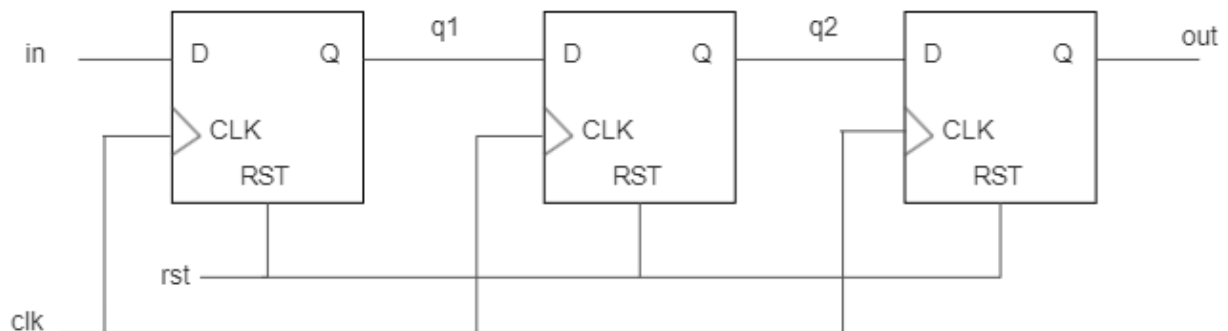always @(posedge clk) begin
    if (rst) begin
        q1 <= 0;
        q2 <= 0;
        out <= 0;
    end
    else begin
        q1 <= in;
        q2 <= q1;
        out <= q2;
    end
end
endmodule
```




```

module reg_blocking2(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        q2 = 0;
        q1 = 0;
        out = 0;
    end
    else begin
        q2 = q1;
        q1 = in;
        out = q2;
    end
end
endmodule

```

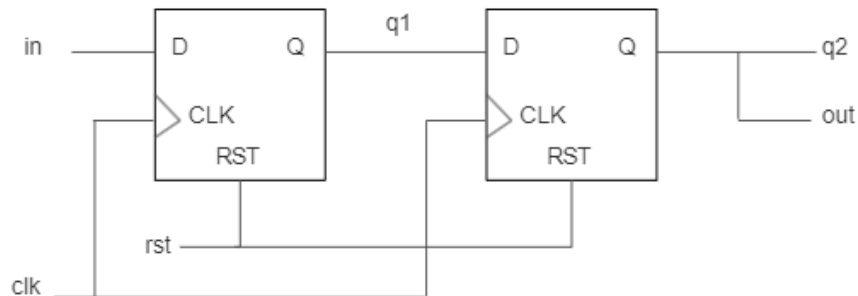


```

module reg_non_blocking2(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        q2 <= 0;
        q1 <= 0;
        out <= 0;
    end
    else begin
        q2 <= q1;
        q1 <= in;
        out <= q2;
    end
end
endmodule

```

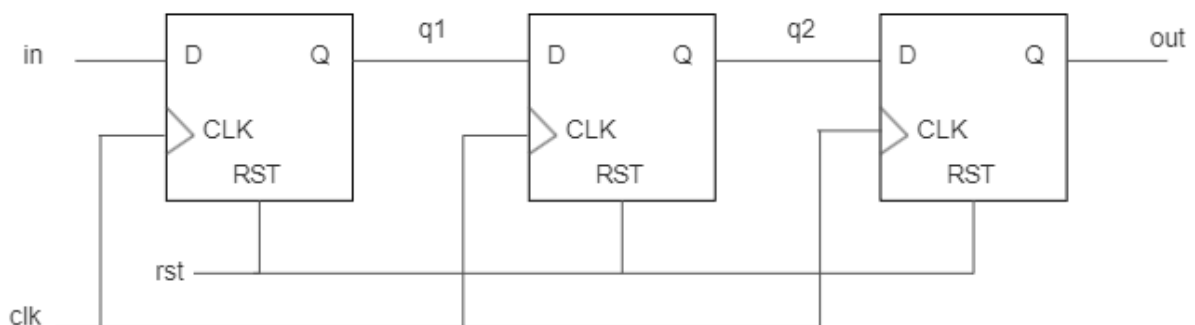


```

module reg_blocking3(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;

always @(posedge clk) begin
    if (rst) begin
        out = 0;
        q2 = 0;
        q1 = 0;
    end
    else begin
        out = q2;
        q2 = q1;
        q1 = in;
    end
end
endmodule

```

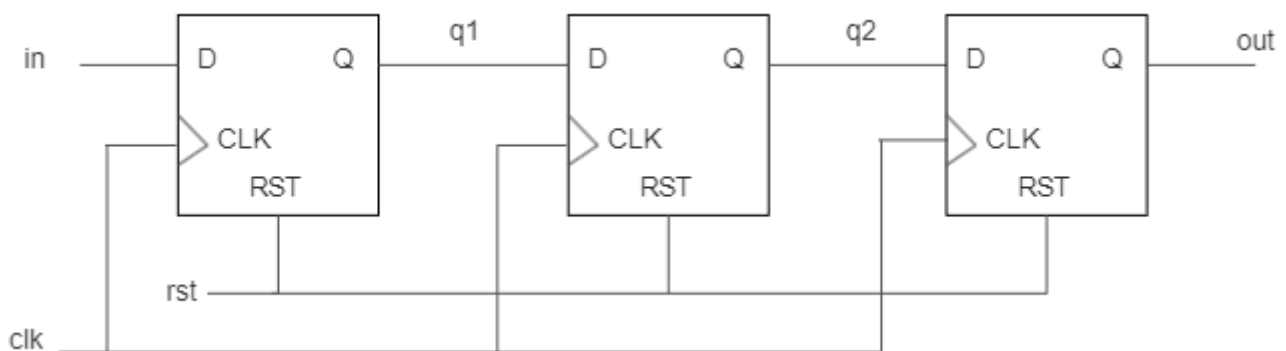


```

module reg_non_blocking3(clk, rst, in, out);
input in, rst, clk;
output reg out;

reg q1, q2;


always @(posedge clk) begin
    if (rst) begin
        out <= 0;
        q2 <= 0;
        q1 <= 0;
    end
    else begin
        out <= q2;
        q2 <= q1;
        q1 <= in;
    end
end
endmodule

```

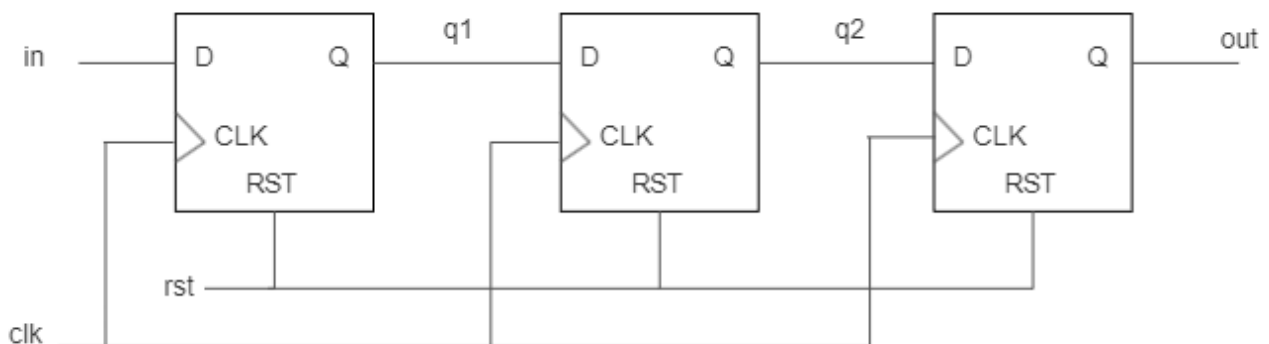


2

```
module comb_blocking1(clk, a, b, c, y);  
input a, b, c, clk;  
output reg y;  
  
reg x;  
  
always @(posedge clk) begin  
    x = a & b;  
    y = x | c;  
end  
  
endmodule
```

 

```
module comb_non_blocking1(clk, a, b, c, y);  
input a, b, c, clk;  
output reg y;  
  
reg x;  
  
always @(posedge clk) begin  
    x <= a & b;  
    y <= x | c;  
end  
  
endmodule
```

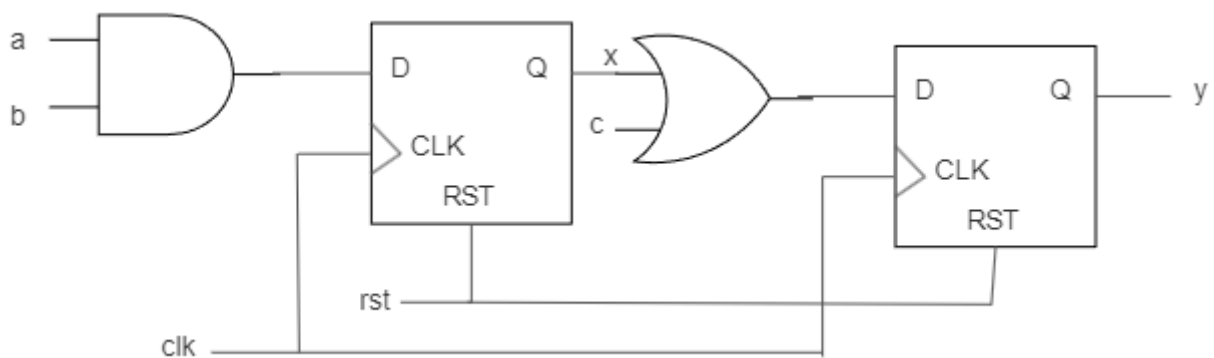

```


module comb_blocking2(clk, a, b, c, y);
input a, b, c, clk;
output reg y;

reg x;

always @(posedge clk) begin
    y = x | c;
    x = a & b;
end

endmodule

```

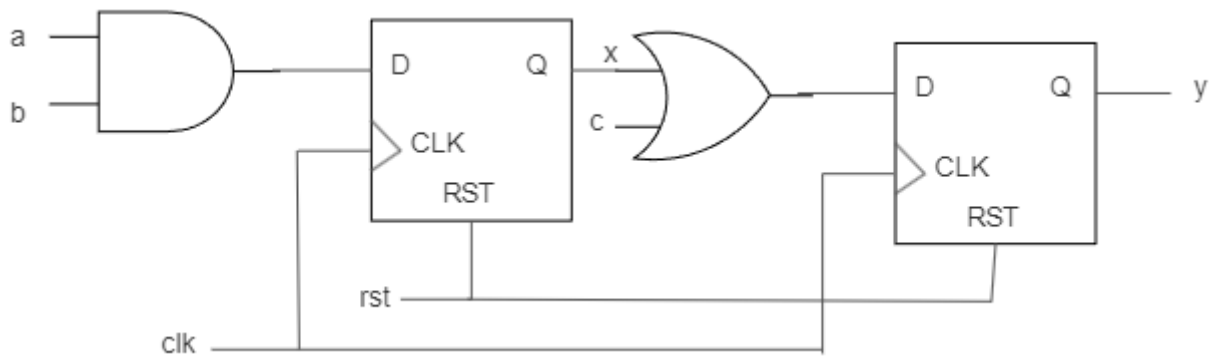

```


module comb_non_blocking2(clk, a, b, c, y);
input a, b, c, clk;
output reg y;

reg x;

always @(posedge clk) begin
    y <= x | c;
    x <= a & b;
end

endmodule

```

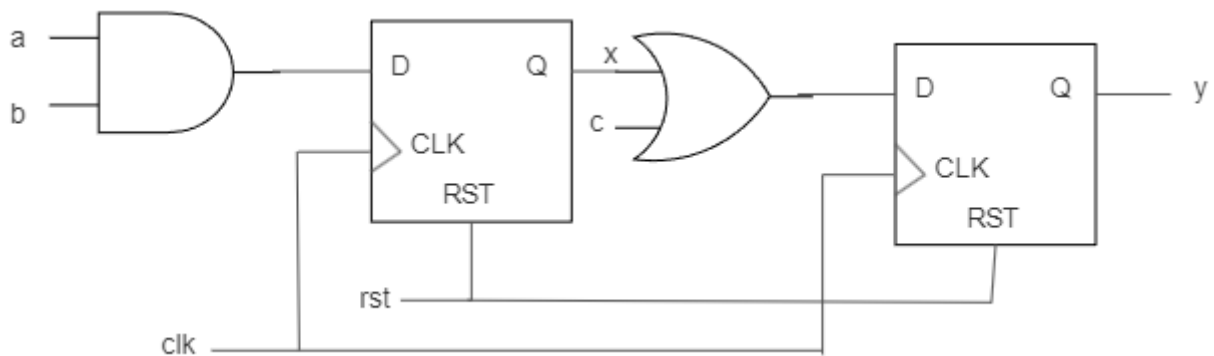

```

module comb_non_blocking3(clk, a, b, c, y);
input a, b, c, clk;
output reg y;


reg x;
reg y_comb;

always @(*) begin
    x = a & b;
    y_comb = x | c;
end

always @(posedge clk) begin
    y <= y_comb;
end

endmodule

```

 

Question 2

SHIFT REGISTER

Verilog Code:

```
module Question2_Ext (clk, rst, load, load_value, PO);

parameter SHIFT_DIRECTION = "LEFT";
parameter SHIFT_AMOUNT = 1;



input clk, rst, load;
input [7:0] load_value;
output reg [7:0] PO;

always @(posedge clk or posedge rst) begin
    if (rst)
        PO <= 0;
    else if (load)
        PO <= load_value;
    else
        case (SHIFT_DIRECTION)
            "LEFT" : PO <= PO << SHIFT_AMOUNT;
                    // PO <= {PO[7 - SHIFT_AMOUNT:0], SHIFT_AMOUNT[1'b0]};
            "RIGHT" : PO <= PO >> SHIFT_AMOUNT;
                    // PO <= {SHIFT_AMOUNT[1'b0], PO[7:SHIFT_AMOUNT]};
        endcase
    end
endmodule
```


Testbench Code 1:

```
module Question2_Ext_tb1 ();
parameter N1 = "LEFT";
parameter N2 = 1;
reg clk, rst, load;
reg [7:0] load_value;
wire [7:0] po;
Question2_Ext #(.SHIFT_DIRECTION(N1),.SHIFT_AMOUNT(N2))
DUT(.clk(clk),.rst(rst),.load(load),.load_value(load_value),.PO(po));
initial begin
    clk = 0;
    forever
        #25 clk = ~clk;
end
initial begin
    rst = 1;
    repeat (10) begin
        load = $random;
        load_value = $random;
        @(negedge clk);
        if (po != 0) begin
            $display("The Shift Register Design is Wrong! ");
            $stop;
        end
    end
    rst = 0; load = 1;
    repeat (10) begin
        load_value = $random;
        @(negedge clk);
    end
    load = 0;
    repeat (20) @(negedge clk);
    load = 1;
    repeat (10) begin
        load_value = $random;
        @(negedge clk);
    end
    load = 0;
    repeat (20) @(negedge clk);
    $stop;
end
endmodule
```

Waveform 1:

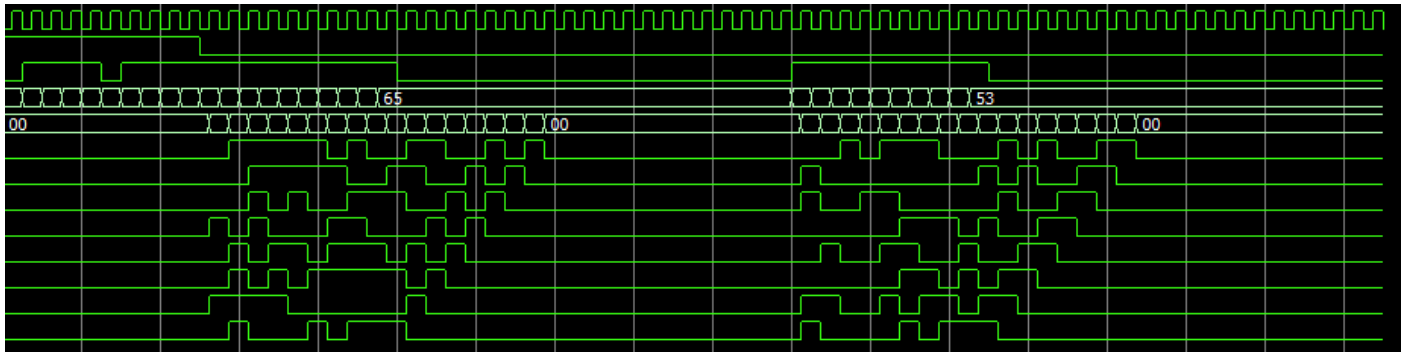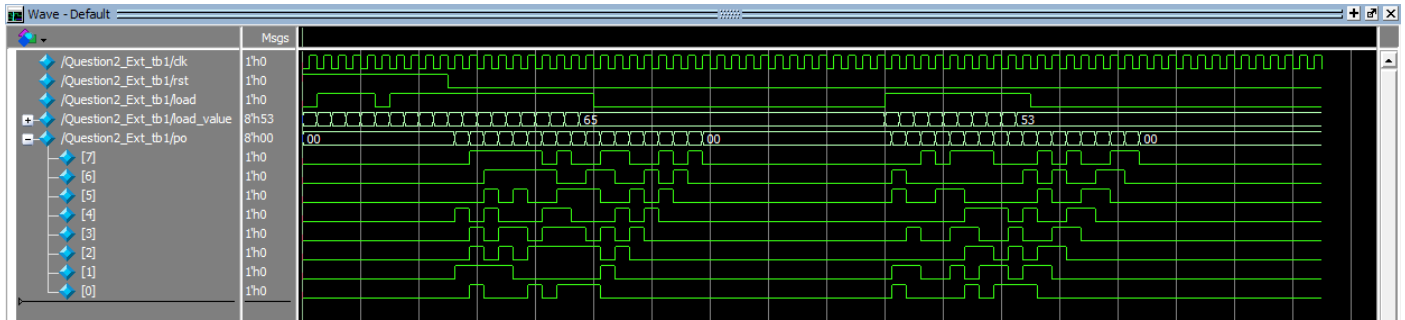



1. Test reset that it forces the output to zero
2. Load signal to load a randomized value to the output
3. Test the shifting operation on the output
4. Load another randomized value to the output
5. Test the shifting again

Testbench Code 2:

```
module Question2_Ext_tb2();

parameter N3 = "RIGHT";
parameter N4 = 2;
reg clk, rst, load;
reg [7:0] load_value;
wire [7:0] po;
Question2_Ext #(.SHIFT_DIRECTION(N3),.SHIFT_AMOUNT(N4))
DUT(.clk(clk),.rst(rst),.load(load),.load_value(load_value),.PO(po));
initial begin
    clk = 0;
    forever
        #25 clk = ~clk;
End
initial begin
    rst = 1;
    repeat (10) begin
        load = $random;
        load_value = $random;
        @(negedge clk);
        if (po != 0) begin
            $display("The Shift Register Design is Wrong!");
            $stop;
        end
    end
    rst = 0; load = 1;
    repeat (10) begin
        load_value = $random;
        @(negedge clk);
    end
    load = 0;
    repeat (20) @(negedge clk);
    load = 1;
    repeat (10) begin
        load_value = $random;
        @(negedge clk);
    end
    load = 0;
    repeat (20) @(negedge clk);
    $stop;
end
endmodule
```

Waveform 2:

  

1. Test reset that it forces the output to zero
2. Load signal to load a randomized value to the output
3. Test the shifting operation on the output
4. Load another randomized value to the output
5. Test the shifting again

Question 3

GRAY COUNTER

Verilog Code:

```
module Question3_Ext (clk, rst, gray_out);  
  
input clk, rst;  
output [1:0] gray_out;  
  
reg [1:0] binary_cnt;  
  
always @(posedge clk or posedge rst) begin  
    if (rst)  
        binary_cnt <= 0;  
    else begin  
        binary_cnt <= binary_cnt + 1;  
    end  
end  
  
assign gray_out[1] = binary_cnt[1];  
assign gray_out[0] = ^binary_cnt;  
  
endmodule
```

Testbench Code:

```
module Question3_Ext_tb();

reg clk, rst;
wire [1:0] gray_out;





Question3_Ext DUT(.clk(clk),.rst(rst),.gray_out(gray_out));

initial begin
clk = 0;
forever
#25 clk = ~clk;
end

initial begin
// initialize all Stimulus Signals
rst = 1;
////////////////////////////////////
// Test Async Signals //
////////////////////////////////////
repeat (20) begin
@(negedge clk);
if (gray_out != 0) begin
$display("Async Control Signals – Q output is not Correct");
$stop;
end
end
////////////////////////////////////
// Test Gray Counter Output – Check Waveform //
////////////////////////////////////
rst = 0;
repeat (100) @(negedge clk);
$stop;
end

endmodule
```

Waveform:

    

1. rst to force output to zero
2. remove reset and check the gray pattern from the waveform