



# **Verilog HDL**

## **Assignment 1 Extended**


By: Magdy Ahmed Abbas Abdelhamid

## Question 1

### Verilog Code:

```
module in1out1 (A, out);  
  
input [3:0] A;  
output out;  
  
assign out = (A > 4'b0010 && A < 4'b1000)? 1'b1 : 1'b0;  
  
endmodule
```

### Waveform:


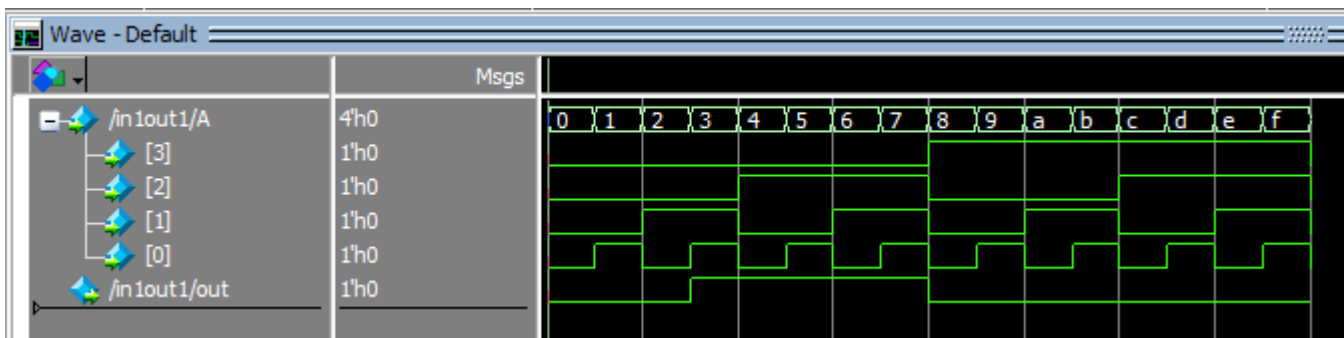


## Question 2

### Verilog Code:

```
module Question2_EXT (A, B, F);  
  
input A, B;  
output F;  
  
assign F = A ^ B;  
  
endmodule
```

### Waveform:

 
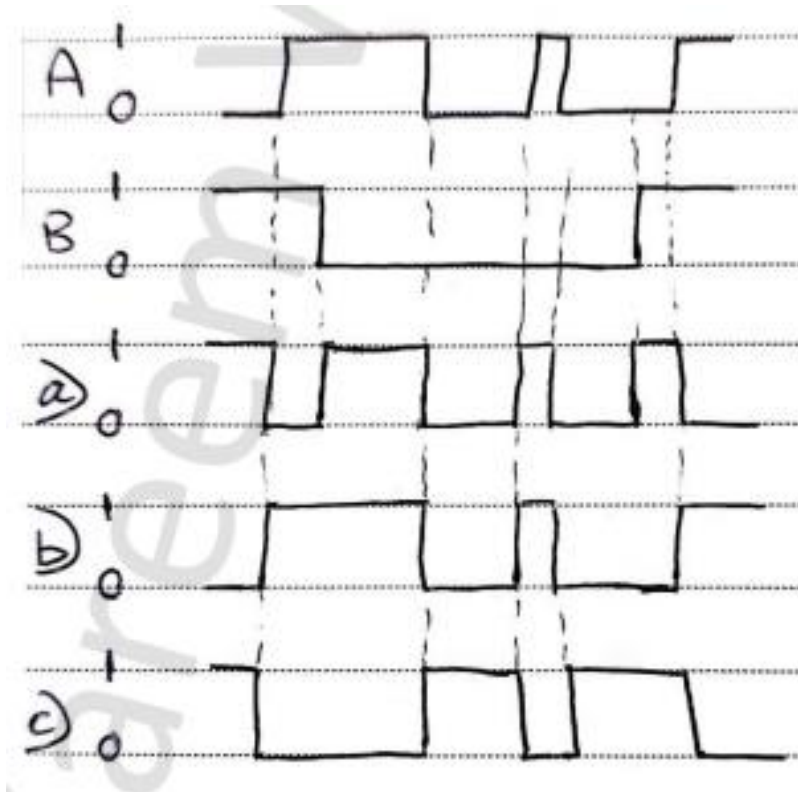


## Question 3

### Verilog Code:

```
module in3out1 (A, B, C, F);  
  
input A, B, C;  
output F;  
  
wire XOR_out, XNOR_out;  
  
assign XOR_out = A ^ B;  
assign XNOR_out = ~(B ^ C);  
  
assign F = XOR_out & XNOR_out & C;  
  
endmodule
```

### Waveform:

 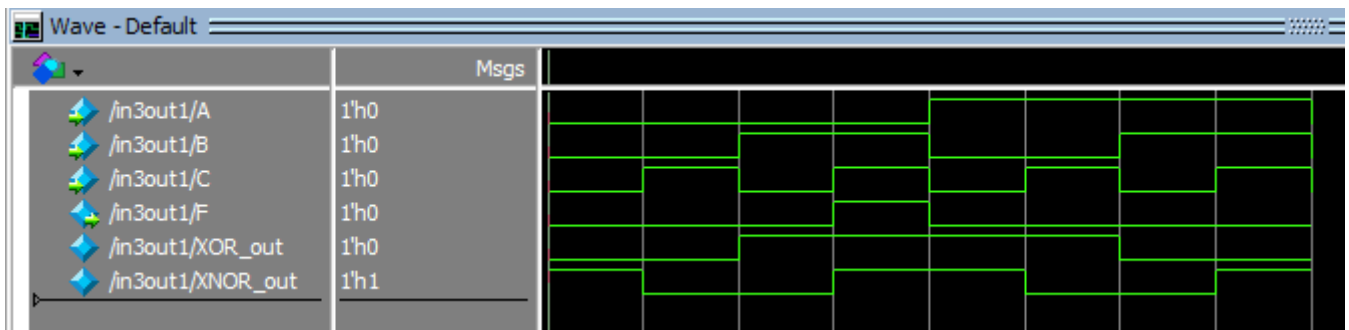


**F = 1 when C is HIGH, B is HIGH, and A is LOW**

## Question 4

### Verilog Code:

```
module prime (A,out);  
  
input [2:0] A;  
output out;  
  
assign out = (~A[2] & A[1]) | (A[2] & A[0]);  
  
endmodule
```

### Waveform:

 


## Question 5

### Verilog Code:

```
module in2out2 (A, B, F, K);  
  
input [3:0] A, B;  
output [3:0] F, K;  
  
assign F = (A >= B)? A : B;  
assign K = (A <= B)? A : B;  
  
endmodule
```

### Waveform:

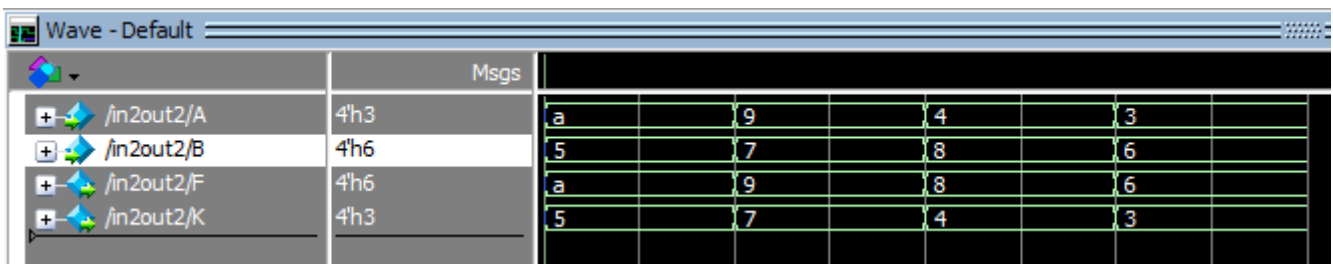


## Question 6

### Verilog Code:

```
module Temperature_Check (Ta, Tb, on);  
  
input [3:0] Ta, Tb;  
output on;  
  
assign on = (Tb <= Ta)? 1'b1 : 1'b0;  
  
endmodule
```

### Waveform:

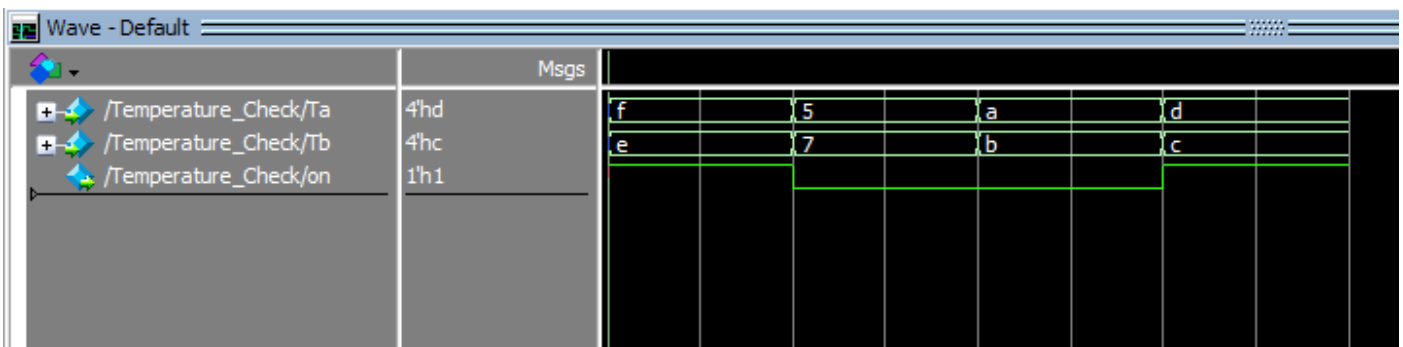

## Question 7

### Verilog Code:

```
module ALU1bit (A, B, Ainvert, Binvert, CarryIn, Operation, CarryOut, Result);  
  
input A, B, Ainvert, Binvert, CarryIn;  
input [1:0] Operation;  
output CarryOut, Result;  
  
wire MUX1_out, MUX2_out, AND_out, OR_out, Adder_out;  
  
assign MUX1_out = (Ainvert == 0)? A : ~A;  
assign MUX2_out = (Binvert == 0)? B : ~B;  
assign AND_out = MUX1_out & MUX2_out;  
assign OR_out = MUX1_out | MUX2_out;  
assign {CarryOut, Adder_out} = MUX1_out + MUX2_out + CarryIn;  
  
assign Result = (Operation == 0)? AND_out : (Operation == 1)? OR_out  
               : Adder_out;  
  
endmodule
```

### Waveform:

